

prob6

October 11, 2016

1 HW6

1.0.1 EECS 16A: Designing Information Devices and Systems I, Fall 2016

1.1 Numpy Calculations

2) a)

```
In [3]: import numpy as np
```

```
A = np.array([[3/20, -1/20],
               [1/20, -7/100]])
b = np.array([[1],[2]])
```

```
v = np.linalg.solve(A,b)
print (v)
```

```
[[ -3.75]
 [-31.25]]
```

2) b)

```
In [4]: import numpy as np
```

```
A = np.array([[1/10 + 1/20 + 1/50, -10, -1/50],
               [0, 1/60 + 1/55, -1/55],
               [-1/50, -1/55, 1/50 + 1/55]])
b = np.array([[1/10 + 1/5], [0], [-1/5]])
```

```
v = np.linalg.solve(A,b)
print(v)
```

```
[[ 10.40226382]
 [  0.14627775]
 [  0.28036569]]
```

4) Verifying with Nodal Analysis

```
In [5]: import numpy as np
```

```
A = np.array([[1/1.5, -1/1.5],
               [-1/1.5, 1/3 + 1/1.5 + 1/3]])
b = np.array([[-1],[-5/3]])
```

```
v = np.linalg.solve(A,b)
print(v)
```

```
[[ -5.5]
 [-4.  ]]
```

1.2 Q6 Circuit solver

In this question we will write a program that solves circuits methodically, able to include both voltage and current sources.

```
In [6]: import numpy as np
        from numpy import linalg
        from __future__ import print_function
```

(i) Write the incidence matrix F for the graph, considering v_1 and v_4 as a combined “supernode”.

```
In [7]: F = np.array([[ -1, 0, 1],
                      [ 1, -1, 0],
                      [ 0, -1, 1],
                      [ 1, 0, -1],
                      [ 0, 1, -1]])

        print('\nF:\n', F)
```

F:

```
[[ -1  0  1]
 [  1 -1  0]
 [  0 -1  1]
 [  1  0 -1]
 [  0  1 -1]]
```

(ii) Specify the resistance matrix R and the vector of voltage sources \vec{b} .

```
In [8]: R1, R2, R3, R4, R5 = 100000, 200, 100, 100000, 100
        Rvec = np.array([R1, R2, R3, R4, R5])
        R = np.eye(5)*Rvec

        Vs = 10
        b = np.array([[Vs], [0], [Vs], [0], [0]])

        # For convenience, we will define the conductance matrix G as the inverse of R.
        G = np.linalg.inv(R)

        print('\nR:\n', R)
        print('\nb:\n', b)
```

R:

```
[[ 100000.    0.    0.    0.    0.]
 [    0.    200.    0.    0.    0.]
 [    0.    0.   100.    0.    0.]
 [    0.    0.    0. 100000.    0.]
 [    0.    0.    0.    0.   100.]]
```

b:

```
[[10]
 [ 0]
 [10]
 [ 0]
 [ 0]]
```

(iii) Write down the vector f so that KCL is satisfied as: $F^T i + f = 0$

```
In [9]: f = np.array([[0], [0], [0]])
        print('\nf:\n', f)
```

```
f:
[[0]
 [0]
 [0]]
```

(iii) What is the rank of F ? Does it have a null space? If so, what is it?

Row-reducing F , we see F has a linearly dependent column (see Problem 6 Part d). Therefore, $\text{rank}(F)$ is 2.

Since it's not a full rank, F does have a null space.

The null space is spanned by $[[1],[1],[1]]$.

In [10]: *# any code you write to help you answer above*

```
from sympy import Matrix
Fm = Matrix(F)

# Frr = row-reduced F matrix
Frr = Fm.rref()
print(Frr)

# Fns = nullspace of F
Fns = Fm.nullspace()
print(Fns)
```

```
(Matrix([
[1.0,  0, -1.0],
[ 0, 1.0, -1.0],
[ 0,  0,  0],
[ 0,  0,  0],
[ 0,  0,  0]]), [0, 1])
(Matrix([
[1.0],
[1.0],
[ 1]]))
```

(iv) Setting a potential in v to 0 corresponds to deleting a column of F . Let $v_4 = 0$, and write down our new “grounded” matrix F : F_{grounded}

```
In [11]: F_ground = F[:, :2]
print('\nF_ground:\n', F_ground)
```

```
F_ground:
[[-1  0]
 [ 1 -1]
 [ 0 -1]
 [ 1  0]
 [ 0  1]]
```

(v) Implement your algebraic solution to compute v in terms of F , G , \vec{f} , and \vec{b} . You may also have to slice \vec{f} and \vec{b} .

```
In [12]: A = np.dot(F_ground.T, np.dot(G, F_ground))
print('\nA:\n', A)

B = np.linalg.inv(A)
```

```

print('\nB:\n', B)

f_gr = f[0:2]

v_gr = - B.dot(f_gr + np.dot(F_grounded.T,np.dot(G,b)))
print('\nv:\n', v_gr)

```

```

A:
[[ 0.00502 -0.005 ]
 [-0.005   0.025 ]]

```

```

B:
[[ 248.75621891  49.75124378]
 [ 49.75124378  49.95024876]]

```

```

v:
[[ 5.]
 [ 5.]]

```

(vi) Compute \vec{i} with your solution of \vec{v} .

```
In [13]: i = G.dot(np.dot(F_grounded, v_gr) + b)
```

```

print('\ni:\n', i)

```

```

i:
[[ 5.00000000e-05]
 [ 8.88178420e-18]
 [ 5.00000000e-02]
 [ 5.00000000e-05]
 [ 5.00000000e-02]]

```

```
In [ ]:
```