

EE 16A: Homework 10

David J. Lee
3031796951
dssd1001@berkeley.edu

November 8, 2016

1. **Worked With...**

Ilya (3031806896), James Zhu (3031793129)

I worked alone on Friday morning, then met up with Ilya and James to discuss on Saturday afternoon.

2. Noise Cancelling Headphones

So we have

$$\begin{bmatrix} S_{ear_left} \\ S_{ear_right} \end{bmatrix} = A \begin{bmatrix} S_{mic1} \\ S_{mic2} \\ S_{mic3} \end{bmatrix} + B \begin{bmatrix} S_{mic1} \\ S_{mic2} \\ S_{mic3} \end{bmatrix} + \begin{bmatrix} S_{left} \\ S_{right} \end{bmatrix},$$

where we define B as the matrix operation implemented by the active noise cancellation circuitry:


Part 1 Build a circuit to drive DAC outputs to the specified $-1.5V$ - $1.5V$ range.

To achieve the goal, we need 3 things:

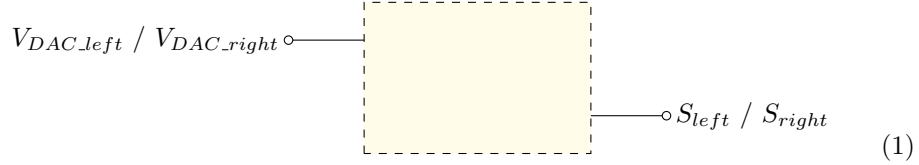
1. Shift the signal($0V - 1V$) to center at $0V$.
2. Provide gain to the signal to go from a $1V$ range to a $3V$ range.

But we already did this in discussion 9B so just use the circuitry from there for both DACs.

We will represent that circuit as like a black box below for later use:



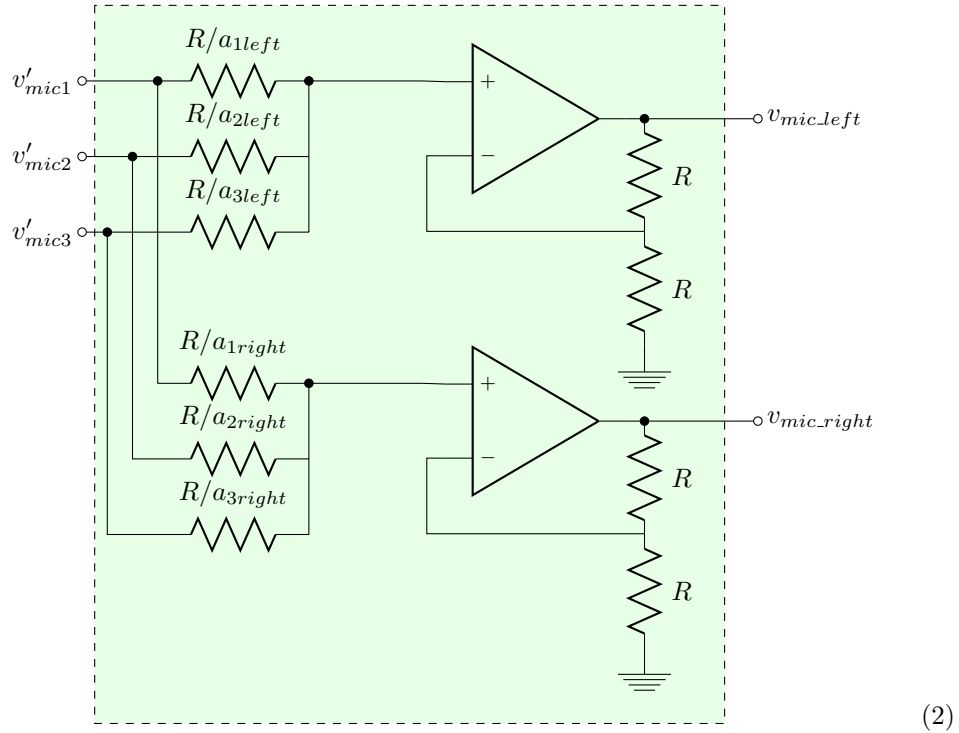
Part 3 Build the mic voltage separation / summer circuitry to implement the matrix operation A :



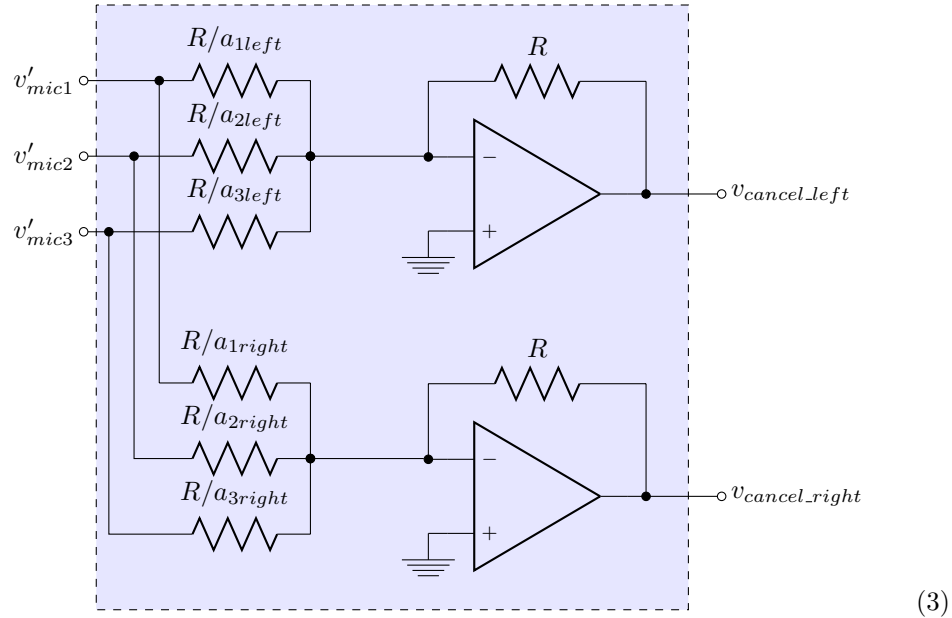
Part 2 Build the external noise canceling circuitry:

In order to ensure that the user doesn't hear any of the sounds picked up by the microphones, we want $B = -A$.

And so we get a circuit that implements B :



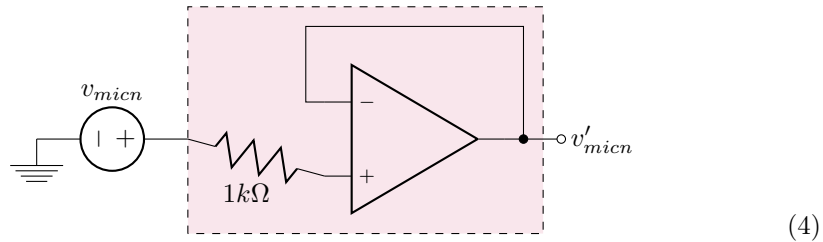for any R , and where each v'_{micn} is connected to the output of each microphone buffer as below:



because we have to take into account the fact that our microphone voltages have source resistances of $1k\Omega$.

Part 4

Now just add a summer for adding in the audio signal/output of all the above circuits for each side to get S_{ear_left} and S_{ear_right} !


The circuit from figure (1) provides

$$\begin{bmatrix} S_{left} \\ S_{right} \end{bmatrix},$$

and the circuits from figures (2) to (4) combined give us

$$A \begin{bmatrix} S_{mic1} \\ S_{mic2} \\ S_{mic3} \end{bmatrix} + B \begin{bmatrix} S_{mic1} \\ S_{mic2} \\ S_{mic3} \end{bmatrix},$$

which would visually look like

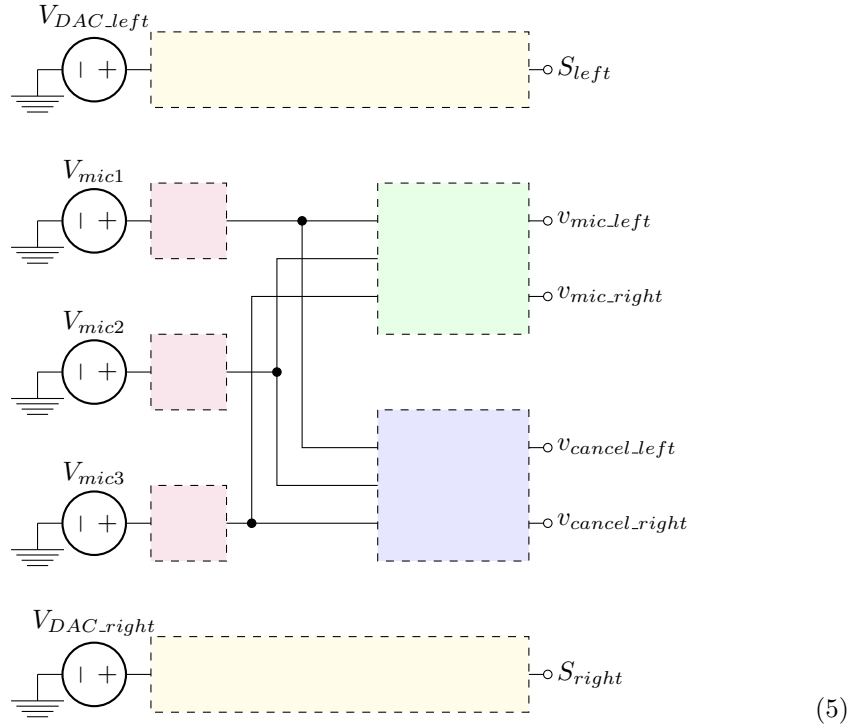

By adding two traditional summers (similar in concept to the green boxes) to the above diagram, we can get

$$S_{ear_left} = v_{mic_left} + v_{cancel_left} + S_{left}$$

$$S_{ear_right} = v_{mic_right} + v_{cancel_right} + S_{right}$$

For example, to get S_{ear_left} ,





where the black box represents the traditional summer.

3. Mechanical: Correlation *see attached iPython notebook*

$$\vec{s}_1 = (1, -1, 1, -1, -1, -1, 1, -1, 1, 1)$$

$$\vec{s}_2 = (1, 2, 3, 4, 5, 6, 7, 6, 5, 4)$$

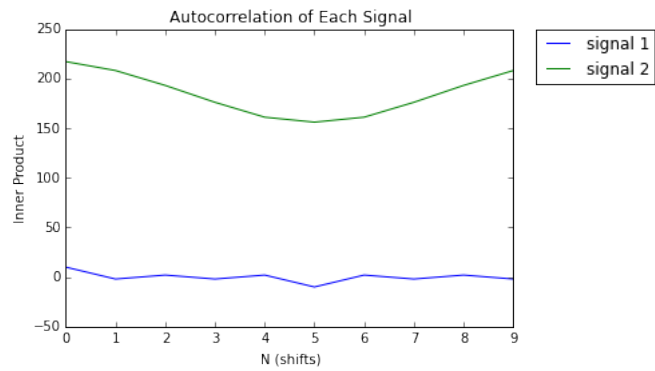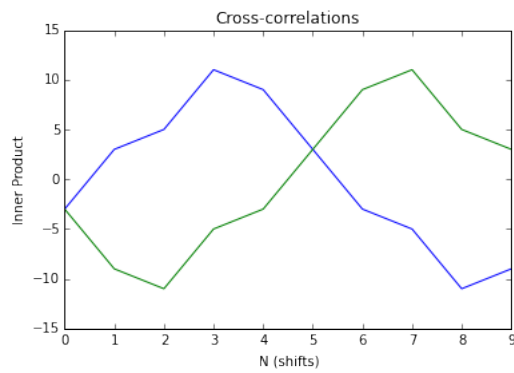(a) *autocorrelation*(b) *cross-correlation*

4. **Inner products** Use the Cauchy-Schwarz inequality to verify (i.e. prove or derive) the triangle inequality:

$$\|\vec{x} + \vec{y}\| \leq \|\vec{x}\| + \|\vec{y}\|.$$

Proof. Observe the following manipulation

$$\begin{aligned}\|x + y\|^2 &= \langle x + y, x + y \rangle \\ &= \langle x, x \rangle + \langle x, y \rangle + \langle y, x \rangle + \langle y, y \rangle \\ &= \|x\|^2 + 2\langle x, y \rangle + \|y\|^2.\end{aligned}$$

Then by the Cauchy-Schwarz inequality we have that

$$\|x + y\|^2 \leq \|x\|^2 + 2\|x\|\|y\| + \|y\|^2 = (\|x\| + \|y\|)^2$$

Thus we have

$$\|x + y\| \leq \|x\| + \|y\|.$$

□

5. Midterm Review

See attached scans

6. **No more circuits :))!!!!** Replicate the projection equation from discussion in LaTeX without the ugly arrows on top like they do in textbooks, which would make Babak happy (not as easy as it sounds)

$$\begin{aligned} \text{proj}_{\mathbf{b}} \mathbf{a} &= \frac{\mathbf{a} \cdot \mathbf{b}}{\|\mathbf{b}\|^2} \mathbf{b} \\ &= \frac{\langle \mathbf{a}, \mathbf{b} \rangle}{\langle \mathbf{b}, \mathbf{b} \rangle} \mathbf{b} \end{aligned}$$

hw10

November 8, 2016

1 2. Mechanical: Correlation

```
In [42]: %pylab inline
import numpy as np
import matplotlib.pyplot as plt
from scipy.linalg import circulant
```

Populating the interactive namespace from numpy and matplotlib

```
In [43]: s1 = np.array([1,-1,1,-1,-1,-1,1,-1,1,1])
s2 = np.array([1,2,3,4,5,6,7,6,5,4])
print("signal 1 = ", s1)
print("signal 2 = ", s2)
```

```
signal 1 = [ 1 -1  1 -1 -1 -1  1 -1  1  1]
signal 2 = [1 2 3 4 5 6 7 6 5 4]
```

1.1 (a) autocorrelation

```
In [46]: c1 = circulant(s1).transpose()
c2 = circulant(s2).transpose()
```


```
In [78]: auto1 = np.dot(c1,s1)
print ("Autocorrelation of signal 1: ", auto1)
auto2 = np.dot(c2,s2)
print ("Autocorrelation of signal 2: ", auto2)
```

```
Autocorrelation of signal 1: [ 10 -2  2 -2  2 -10  2 -2  2 -2]
Autocorrelation of signal 2: [217 208 193 176 161 156 161 176 193 208]
```

```
In [79]: plt.title('Autocorrelation of Each Signal')
plt.plot(auto1, label='signal 1')
plt.plot(auto2, label='signal 2')
plt.xlabel('N (shifts)')
plt.ylabel('Inner Product')

plt.legend(bbox_to_anchor=(1.05, 1), loc=0, borderaxespad=0.)
```
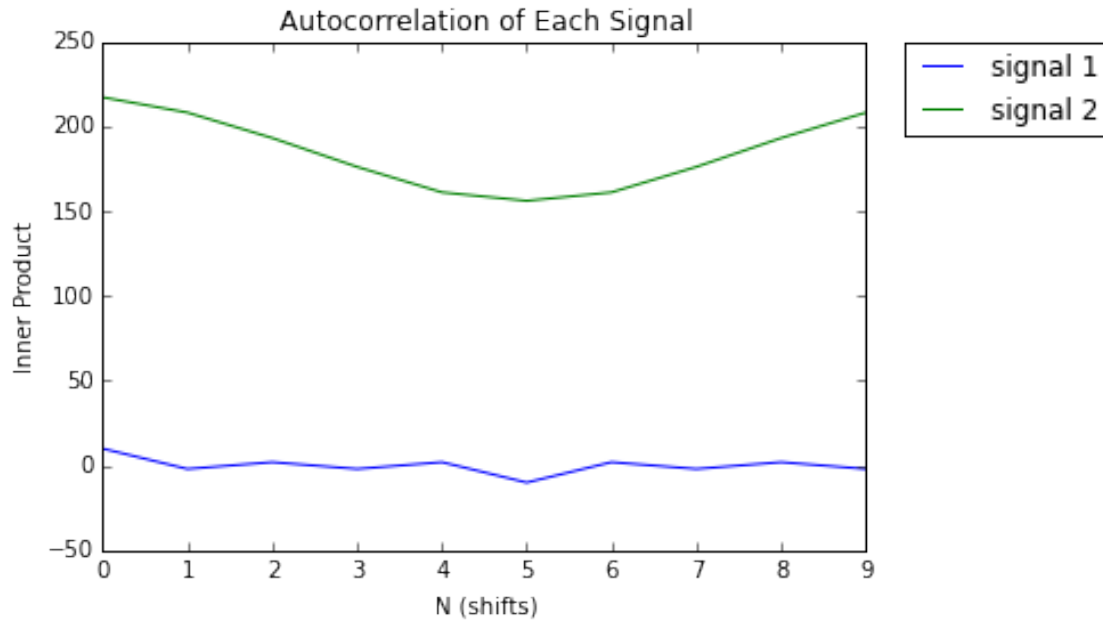
```
Out[79]: <matplotlib.legend.Legend at 0x10c450fd0>
```




1.2 (b) cross-correlation

```
In [77]: cross1 = np.dot(c2,s1)
          print ("Cross-correlation 1: ", cross1)
          cross2 = np.dot(c1,s2)
          print ("Cross-correlation 2: ", cross2)

Cross-correlation 1: [ -3   3   5  11   9   3  -3  -5 -11  -9]
Cross-correlation 2: [ -3  -9 -11  -5  -3   3   9  11   5   3]


In [80]: plt.title('Cross-correlations')
          plt.plot(cross1)
          plt.plot(cross2)
          plt.xlabel('N (shifts)')
          plt.ylabel('Inner Product')

Out[80]: <matplotlib.text.Text at 0x10c461a20>
```

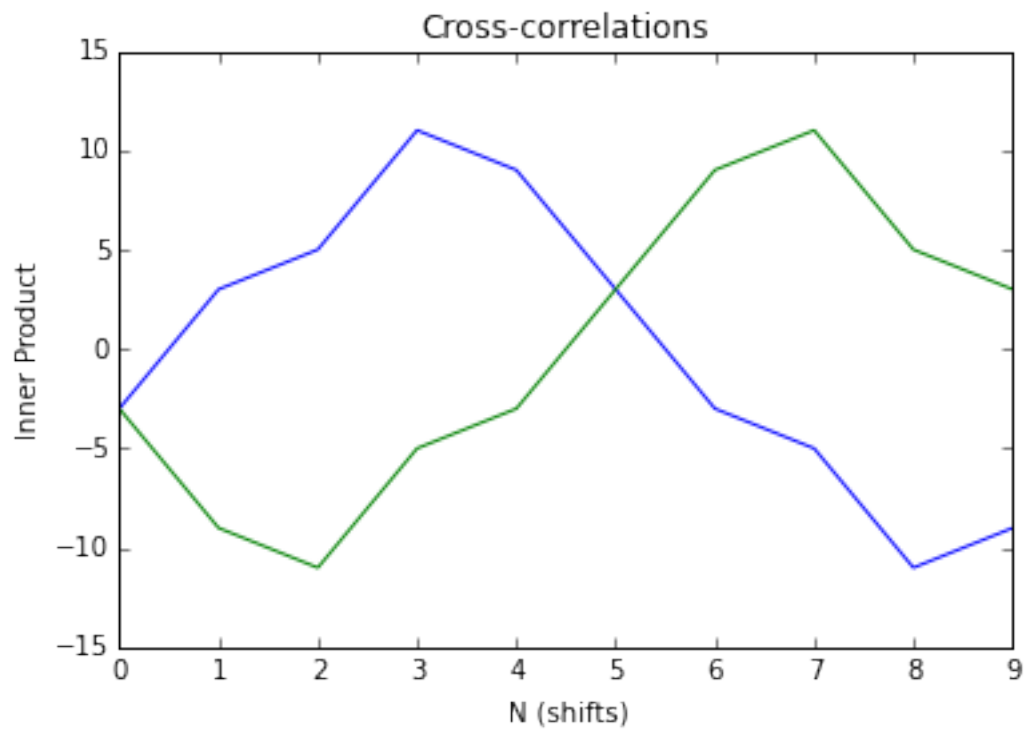


MT3) a) $X \xrightarrow{R_1} B \quad \boxed{R_{eq} = R_1 + (R_2 \parallel (R_3 + R_4))}$

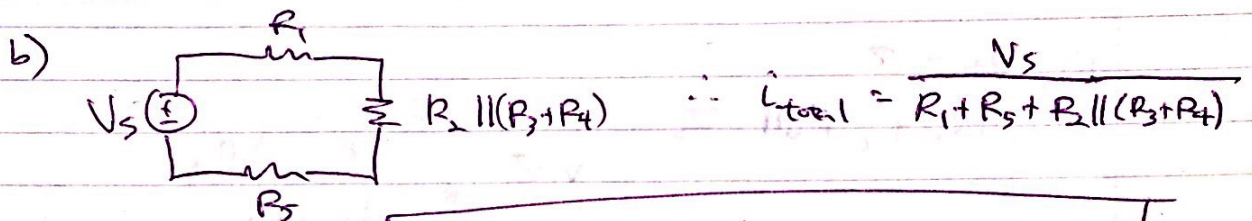As $R_4 \rightarrow \infty$, $\boxed{R_{eq} = R_1 + R_2}$



$\therefore \boxed{I_2 = \frac{R_3 + R_4}{R_2 + R_3 + R_4} \left(\frac{V_s}{R_1 + R_2 + R_2 \parallel (R_3 + R_4)} \right)}$

MT 4)

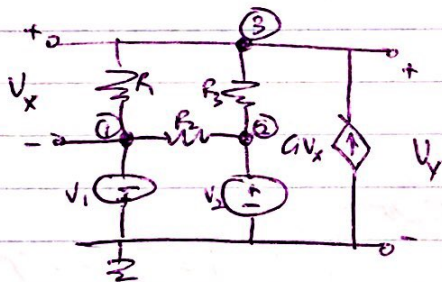

Label nodes ①, ②, ③.

$V_{③} - V_{①} = V_x = V_y - (-V_1)$
 $V_{③} = V_y$
 $V_{①} = -V_1$
 $V_{②} = V_2$
 $V_{y1} = V_x + V_1$

Node Analysis @ ②, ③:

$\frac{V_{③} - V_{①}}{R_1} + \frac{V_{③} - V_{②}}{R_3} + -G V_x = 0$

$\frac{V_{③} - V_{①}}{R_1} + \frac{V_{③} - V_{②}}{R_3} + -G V_x = 0$

$\frac{V_x}{R_1} + \frac{V_y - V_2}{R_3} - G V_x = 0$

$\frac{V_x}{R_1} + \frac{V_x + V_1 - V_2}{R_3} - G V_x = 0$

$\frac{1}{10} V_x + \frac{1}{40} V_x - \frac{1}{4} V_x = 0$


$\frac{4}{40} V_x + \frac{1}{40} V_x - \frac{10}{40} V_x = 0$

$-\frac{1}{8} V_x = 0$

$\boxed{V_x = -8 V} \rightarrow \boxed{V_y = -3 V}$

M45)


9)

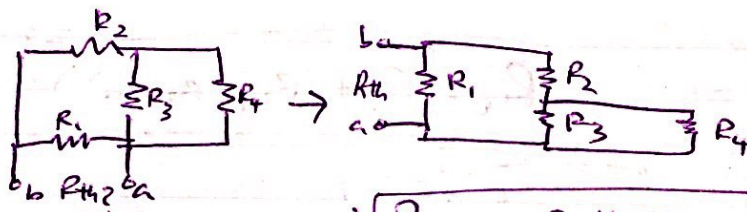


$$\therefore [R_{th} = R_1 \parallel (R_2 + (R_3 \parallel R_4))]$$

b) $V_{th} = ?$


First, null I_s :

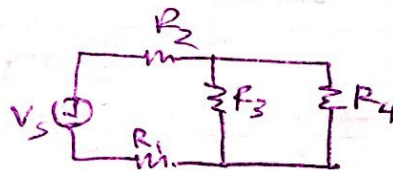
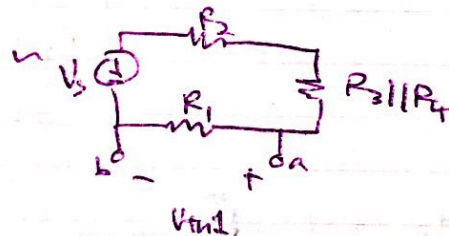
$$\therefore V_{th1} = \frac{R_1}{R_1 + R_2 + (R_3 \parallel R_4)} V_s$$



Next, null V_s :

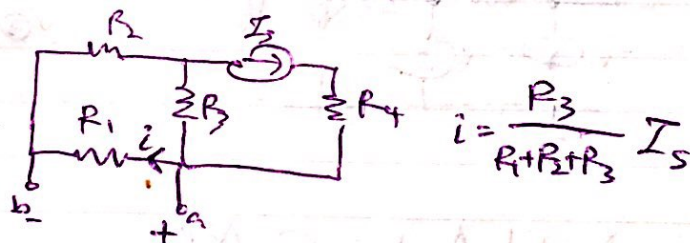


$$i = \frac{R_3}{R_1 + R_2 + R_3} I_s$$

$$V_{th2} = i R_1 = \frac{R_1 R_3}{R_1 + R_2 + R_3} I_s$$

$$\therefore V_{th} = V_{th1} + V_{th2} = \frac{R_1}{R_1 + R_2 + (R_3 \parallel R_4)} V_s + \frac{R_1 R_3}{R_1 + R_2 + R_3} I_s$$

6) a)

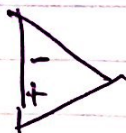

b) From the golden rules, we get

$$V^+ = V^- = V_{in2}$$

And using the knowledge that $I^- = I^+ = 0$,
we can use KVL to perform nodal analysis
@ the V^- node:

$$\frac{V_{in2} - V_{in1}}{2} + \frac{V_{in2} - V_o}{6} = 0$$

$$\frac{V_o - V_{in2}}{3} = \frac{3(V_{in2} - V_{in1})}{6} \Rightarrow \underline{V_o = 4V_{in2} - 3V_{in1}}$$

7)

a)

$$F = \begin{bmatrix} 1 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix}$$

b) Put F into RREF:

$$\begin{bmatrix} 1 & 0 & -1 \\ 0 & 1 & -1 \\ 0 & -1 & 1 \end{bmatrix} \sim \begin{bmatrix} 1 & 0 & -1 \\ 0 & 1 & -1 \\ 0 & 0 & 0 \end{bmatrix}$$


We can easily see that there are 2 lin. independent cols,

$$\therefore \underline{\text{rank}(F) = 2}$$

To get null space, solve for $Fx = 0$


$$1 \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} + 1 \begin{bmatrix} 0 \\ 1 \\ 0 \end{bmatrix} + 1 \begin{bmatrix} -1 \\ -1 \\ 1 \end{bmatrix} = 0$$
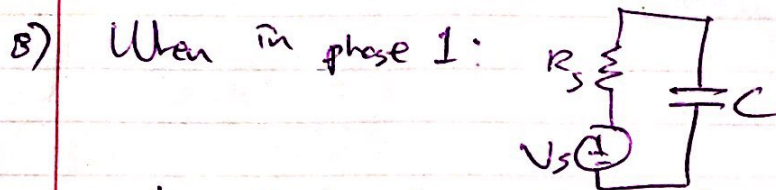
$$\therefore \underline{\begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} \text{ is the basis of } N(F)}$$





At steady state, C is charged to V_s ,
so $Q_c = CV_s$

In phase 2:

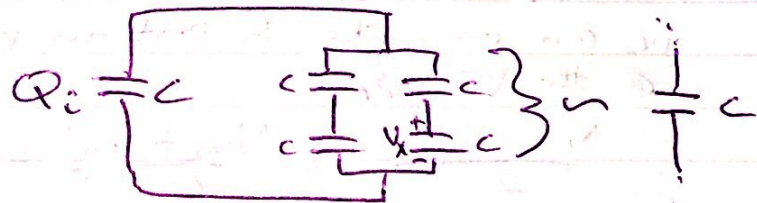


Due to charge sharing, and conservation of charge,
on each side there is $Q_c/2$ charges.
That means that on each of the four capacitors
on the right, there are $Q_c/4$ charges.
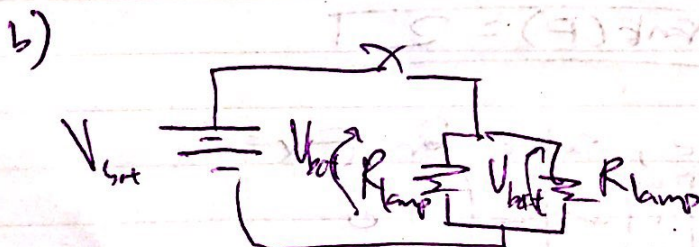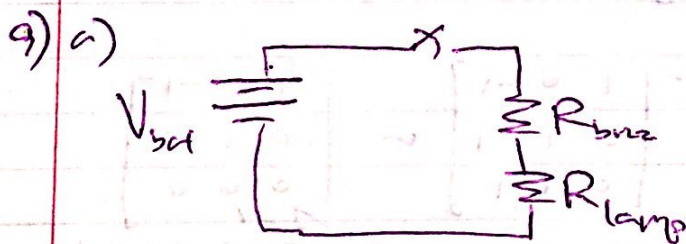
$$\therefore V_x = \frac{Q}{C} = \boxed{\frac{Q_c}{4C}}$$



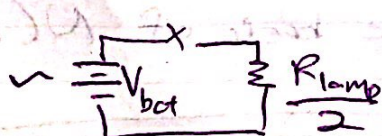Between the choice of
putting the lamps in
series or parallel,
I would put them in
parallel to maximize power
dissipated.




$$\therefore I = \frac{2V_{bot}}{R_{lamp}}$$

$$\therefore P = IV = \boxed{\frac{2(V_{bot})^2}{R_{lamp}}}$$

$$10) a) \frac{V_{out} - V_1}{R_1} + \frac{V_{out} - V_2}{R_2} + \frac{V_{out} - V_3}{R_3} = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_{out} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$
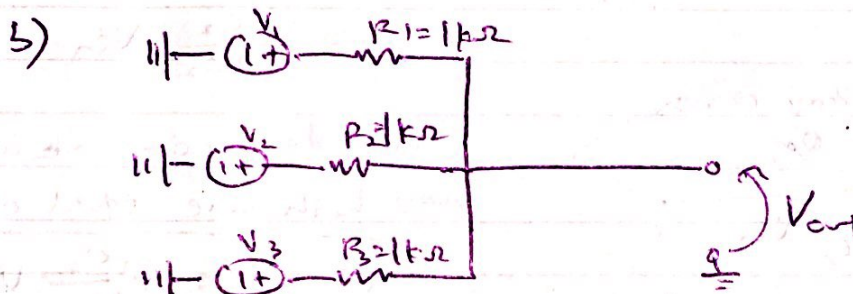
$$V_{out} = (R_1 \parallel R_2 \parallel R_3) \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$




$$\therefore V_{out} = \frac{1}{R} (V_1 + V_2 + \dots + V_n)$$

which in this case is

$$V_{out} = \frac{1}{3} (V_1 + V_2 + V_3)$$

c) the gain is $\frac{10 \mu V}{2.5 V} \times \frac{2.5 V}{0.01 V} = \times 250$



We can use :

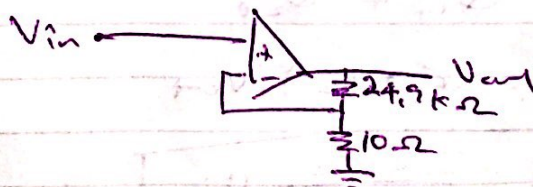

$$\therefore V_{out} = \left(1 + \frac{24.9k\Omega}{10\Omega} \right) V_{in}$$

$$V_{out} = 250 V_{in}$$

ii) a) in phase I:

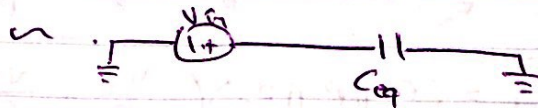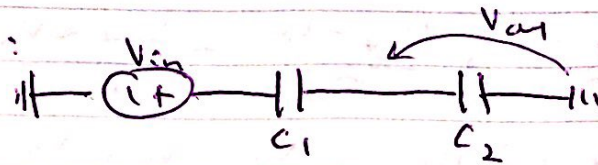

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\therefore Q_c = C_{eq} V_{in}$$

$$= \frac{C_1 C_2}{C_1 + C_2} V_{in}$$

To find voltage across each, $V_n = Q/C_n$

$$\boxed{V_1 = \frac{C_2}{C_1 + C_2} V_{in}}$$

$$\boxed{V_2 = \frac{C_1}{C_1 + C_2} V_{in}}$$

Since the capacitors are in series, they both have equal charge of

$$\boxed{Q_1 = Q_2 = \frac{C_1 C_2}{C_1 + C_2} V_{in}}$$

b) In phase 2:



As a function of V_{out} , C_1 & C_2 ,

$$\cancel{Q_1 = Q_2} = \boxed{Q_1 = C_1 V_{out}, \quad Q_2 = C_2 V_{out}}$$

c) $Q_c = Q_f$

$$Q_{1,2} + Q_{2,2} = Q_{1,f} + Q_{2,f}$$

$$\frac{2 C_1 C_2}{C_1 + C_2} V_{in} = (C_1 + C_2) V_{out}$$

$$\therefore \boxed{V_{out} = \frac{2 C_1 C_2}{(C_1 + C_2)^2} V_{in}}$$

d) Efficiency = E_2 / E_1

$$= \frac{\cancel{C} \left(\frac{V_{in}}{2} \right)^2}{C \left(\frac{V_{in}}{2} \right)^2}$$

$$= \boxed{1}$$