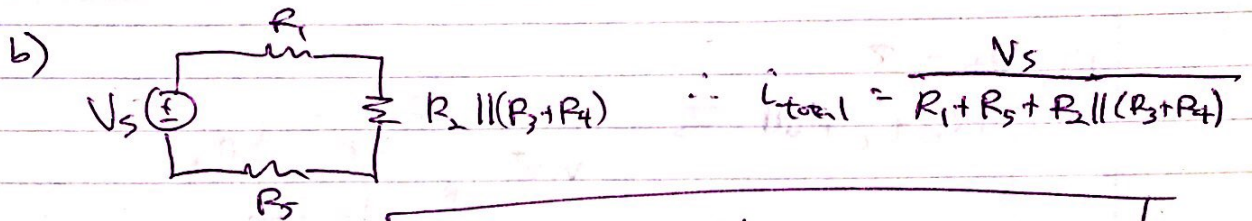



MT3) a)  $X \xrightarrow{R_1} B \quad \boxed{R_{eq} = R_1 + (R_2 \parallel (R_3 + R_4))}$

As  $R_4 \rightarrow \infty$ ,  $\boxed{R_{eq} = R_1 + R_2}$



$\therefore \boxed{I_2 = \frac{R_3 + R_4}{R_2 + R_3 + R_4} \left( \frac{V_s}{R_1 + R_5 + R_2 \parallel (R_3 + R_4)} \right)}$

MT 4)

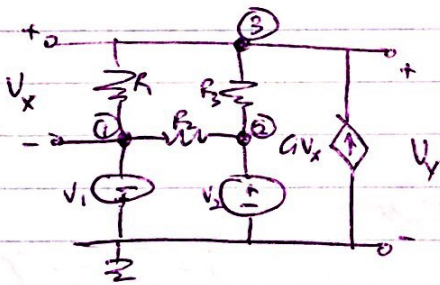

Label nodes ①, ②, ③.

$$\begin{aligned} V_{③} - V_{①} &= V_x = V_y - (-V_1) \\ V_{③} &= V_y \\ V_{①} &= -V_1 \\ V_{②} &= V_2 \\ V_{y1} &= V_x + V_1 \end{aligned}$$

Node Analysis @ ①, ②, ③:

$$\frac{V_{③} - V_{①}}{R_1} + \frac{V_{③} - V_{②}}{R_3} + -G V_x = 0$$

$$\frac{V_{③} - V_{①}}{R_1} + \frac{V_{③} - V_{②}}{R_3} + -G V_x = 0$$

$$\frac{V_x}{R_1} + \frac{V_y - V_2}{R_3} - G V_x = 0$$

$$\frac{V_x}{R_1} + \frac{V_x + V_1 - V_2}{R_3} - G V_x = 0$$

$$\frac{1}{10} V_x + \frac{1}{40} V_x - \frac{1}{4} V_x = 0$$

$$\frac{4}{40} V_x + \frac{1}{40} V_x - \frac{10}{40} V_x = 0$$


$$-\frac{1}{8} V_x = 0$$

$$\boxed{V_x = -8 \text{ V}} \rightarrow \boxed{V_y = -3 \text{ V}}$$



M45)


9)

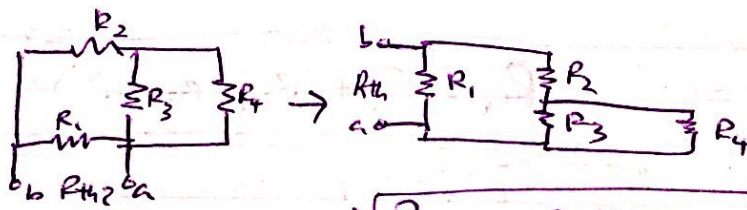


$$\therefore [R_{th} = R_1 \parallel (R_2 + (R_3 \parallel R_4))]$$

b)  $V_{th} = ?$


First, null  $I_s$ :

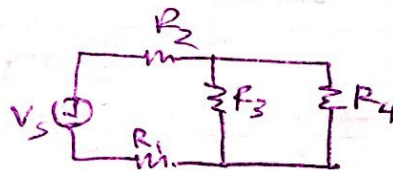
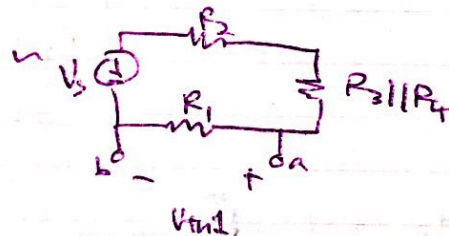
$$\therefore V_{th1} = \frac{R_1}{R_1 + R_2 + (R_3 \parallel R_4)} V_s$$



Next, null  $V_s$ :

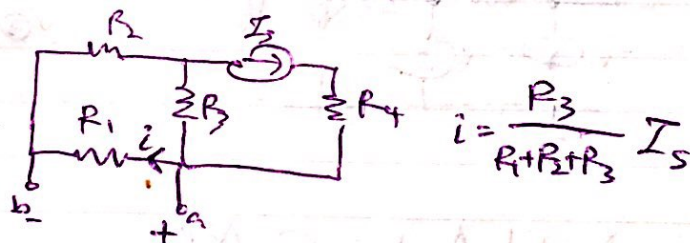


$$i = \frac{R_3}{R_1 + R_2 + R_3} I_s$$

$$V_{th2} = i R_1 = \frac{R_1 R_3}{R_1 + R_2 + R_3} I_s$$

$$\therefore V_{th} = V_{th1} + V_{th2} = \frac{R_1}{R_1 + R_2 + (R_3 \parallel R_4)} V_s + \frac{R_1 R_3}{R_1 + R_2 + R_3} I_s$$



6) a)

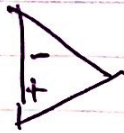

b) From the golden rules, we get

$$V^+ = V^- = V_{in2}$$

And using the knowledge that  $I^- = I^+ = 0$ , we can use KVL to perform nodal analysis @ the  $V^-$  node:

$$\frac{V_{in2} - V_{in1}}{2} + \frac{V_{in2} - V_o}{6} = 0$$

$$\frac{V_o - V_{in2}}{6} = \frac{3(V_{in2} - V_{in1})}{6} \quad \therefore \underline{V_o = 4V_{in2} - 3V_{in1}}$$

7)

a)  $F = \begin{bmatrix} 1 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix}$

b) Put  $F$  into RREF:  $\begin{bmatrix} 1 & 0 & -1 \\ 0 & 1 & -1 \\ 0 & -1 & 1 \end{bmatrix} \sim \begin{bmatrix} 1 & 0 & -1 \\ 0 & 1 & -1 \\ 0 & 0 & 0 \end{bmatrix}$


We can easily see that there are 2 lin. independent cols,  
 $\therefore \underline{\text{rank}(F) = 2}$

To get null space, solve for  $Fx = 0$

$$1 \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} + 1 \begin{bmatrix} 0 \\ 1 \\ 0 \end{bmatrix} + 1 \begin{bmatrix} -1 \\ -1 \\ 1 \end{bmatrix} = 0$$

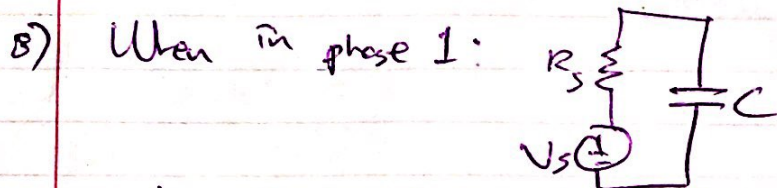
$$\therefore \underline{\begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} \text{ is the basis of } N(F)}$$







At steady state,  $C$  is charged to  $V_s$ ,  
so  $Q_c = CV_s$

In phase 2:

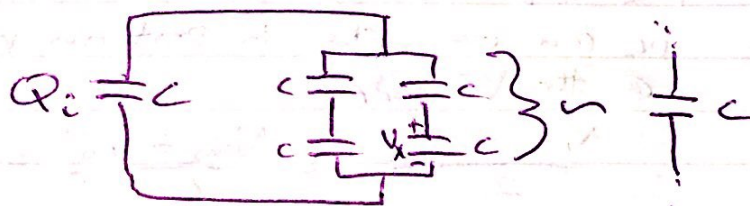


Due to charge sharing, and conservation of charge,  
on each side there is  $Q_c/2$  charges.  
That means that on each of the four capacitors  
on the right, there are  $Q_c/4$  charges.
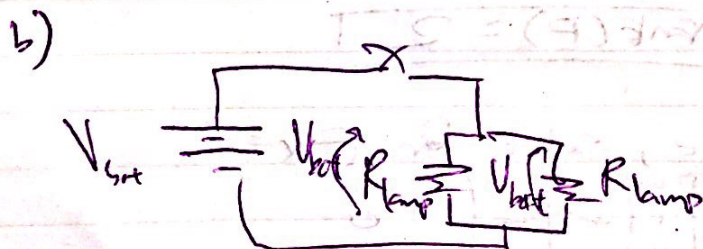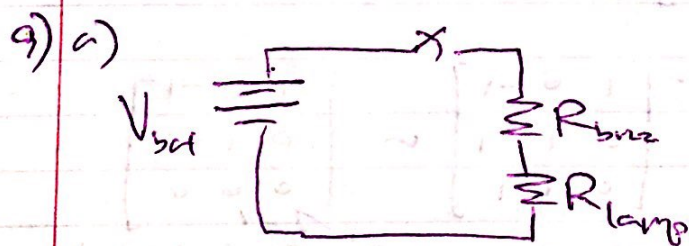
$$\therefore V_x = \frac{Q}{C} = \boxed{\frac{Q_c}{4C}}$$



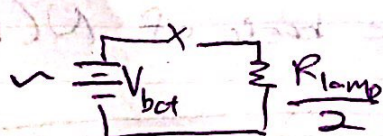Between the choice of  
putting the lamps in  
series or parallel,  
I would put them in  
parallel to maximize power  
dissipated.



$$\therefore I = \frac{2V_{bot}}{R_{lamp}}$$


$$\therefore P = IV = \boxed{\frac{2(V_{bot})^2}{R_{lamp}}}$$



$$10) a) \frac{V_{out} - V_1}{R_1} + \frac{V_{out} - V_2}{R_2} + \frac{V_{out} - V_3}{R_3} = 0$$

$$\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_{out} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$
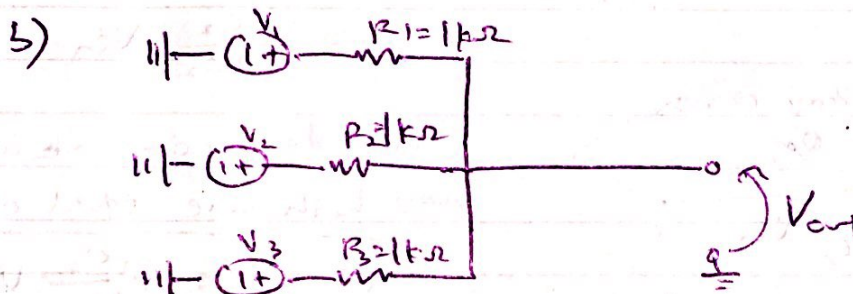
$$V_{out} = (R_1 \parallel R_2 \parallel R_3) \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$




$$\therefore V_{out} = \frac{1}{R} (V_1 + V_2 + \dots + V_n)$$

which in this case is

$$V_{out} = \frac{1}{3} (V_1 + V_2 + V_3)$$

c) the gain is  $\frac{10 \mu V}{2.5 V} \div \frac{2.5 V}{0.01 V} = \times 250$

We can use :


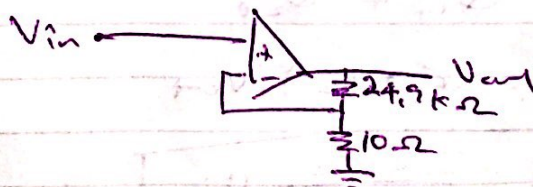


$$\therefore V_{out} = \left( 1 + \frac{24.9k\Omega}{10\Omega} \right) V_{in}$$

$$V_{out} = 250 V_{in}$$



ii) a) in phase I:

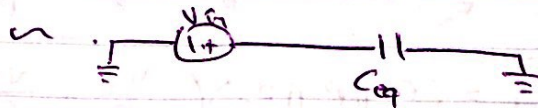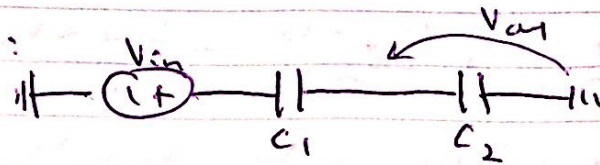

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\therefore Q_c = C_{eq} V_{in}$$

$$= \frac{C_1 C_2}{C_1 + C_2} V_{in}$$

To find voltage across each,  $V_n = Q/C_n$


$$\boxed{V_1 = \frac{C_2}{C_1 + C_2} V_{in}}$$

$$\boxed{V_2 = \frac{C_1}{C_1 + C_2} V_{in}}$$

Since the capacitors are in series, they both have equal charge of

$$\boxed{Q_1 = Q_2 = \frac{C_1 C_2}{C_1 + C_2} V_{in}}$$

b) In phase 2:

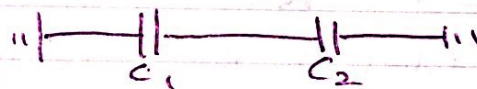

As a function of  $V_{out}$ ,  $C_1$  &  $C_2$ ,

$$\cancel{Q_1 = Q_2} = \boxed{Q_1 = C_1 V_{out}, \quad Q_2 = C_2 V_{out}}$$

c)  $Q_c = Q_f$

$$Q_{1,2} + Q_{2,2} = Q_{1,f} + Q_{2,f}$$

$$\frac{2 C_1 C_2}{C_1 + C_2} V_{in} = (C_1 + C_2) V_{out}$$

$$\therefore \boxed{V_{out} = \frac{2 C_1 C_2}{(C_1 + C_2)^2} V_{in}}$$

d) Efficiency =  $E_2 / E_1$

$$= \frac{\cancel{C} \left( \frac{V_{in}}{2} \right)^2}{C \left( \frac{V_{in}}{2} \right)^2}$$

$$= \boxed{1}$$