



EE 16A HW 7

DAVID Lee
3031796951



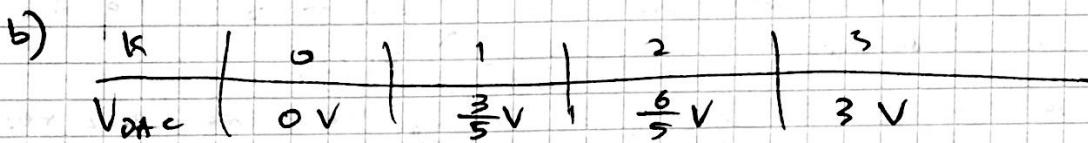
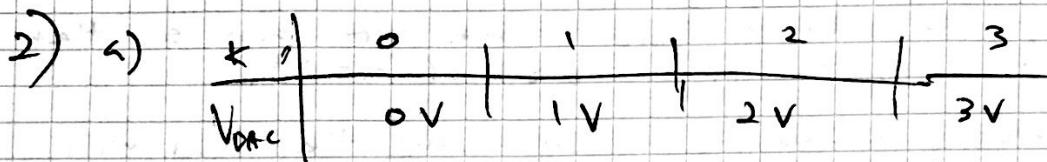
i) MATTHEW SOH - 3032109159

WILLIAM SOH - 3031799759

I worked alone for 5 hours then met up with the other two to discuss our approaches to each problem.



Thevenin Equivalents:

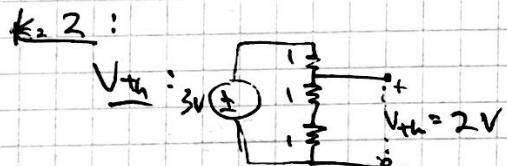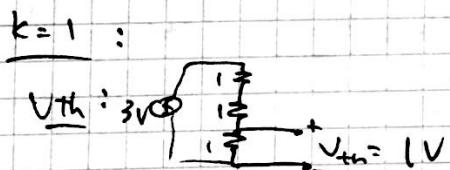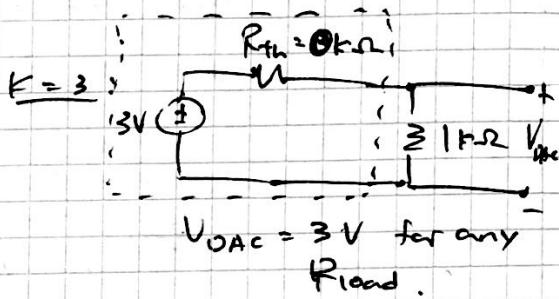
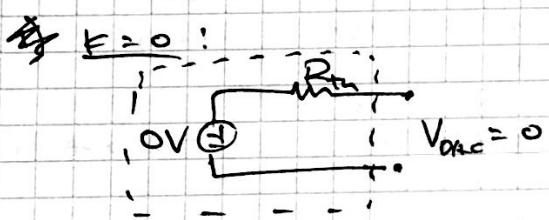


$R_{th} :$

$$R_{th} = \frac{R_2 + 2k\Omega}{R_1 + \frac{1}{k\Omega}} = \frac{(R_1 || R_2)}{\frac{1}{k\Omega} + \frac{1}{2k}} = \frac{2}{3}k\Omega$$

$R_{th} :$

$$R_{th} = \frac{2}{3}k\Omega$$

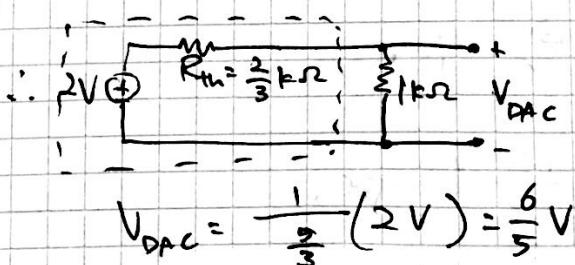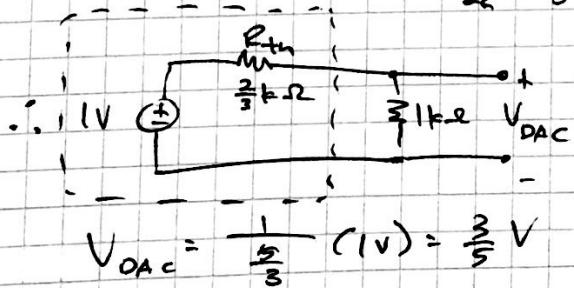

c) Only two entries ($k=1$ & $k=2$) are different those are the positions of a voltage divider. Because of this, R_{load} affects the ideal V_{DAC} @ only these places.

d) Since the R_{load} of $1\text{k}\Omega$ altered @ $k=1$ & $k=2$ (switches 1 & 2), first try modifying those circuits only.

Looking back @ my Thévenin equivalents from part b), one way of achieving the ideal V_{DAC} 's is to modify the design so that $R_{th} \rightarrow 0$ (Case 1). Another way ~~is~~ would be to modify the design so that the value of R_{load} becomes very large so that in the calculation for V_{DAC} , the R_{th} is negligible (Case 2).



Case 1 seems easily achievable if we assume that R_{load} will always be $1\text{k}\Omega$, for we can just modify so that R_{th} is just significantly smaller than $1\text{k}\Omega$ - to make the ratio of voltage divider ($\frac{R_{load}}{R_{load} + R_{th}}$) ≈ 1 .

We can do this simply by setting the three $1\text{k}\Omega$ resistors in a series to $10\text{k}\Omega$ (or anything small but equal to each other so that the voltage differences are kept).

When the three resistors are now $10\text{k}\Omega$,

$$V_{DAC}|_{k=0} = 0V, V_{DAC}|_{k=3} = 3V,$$

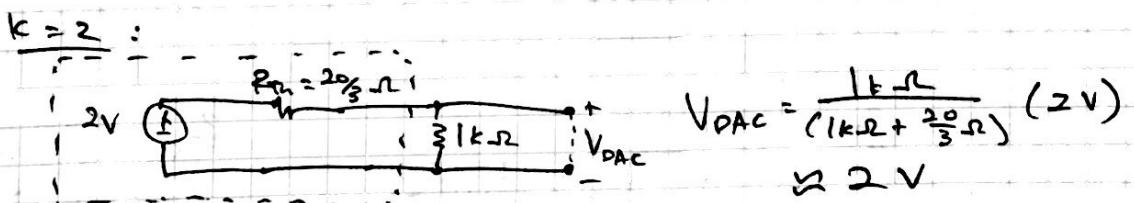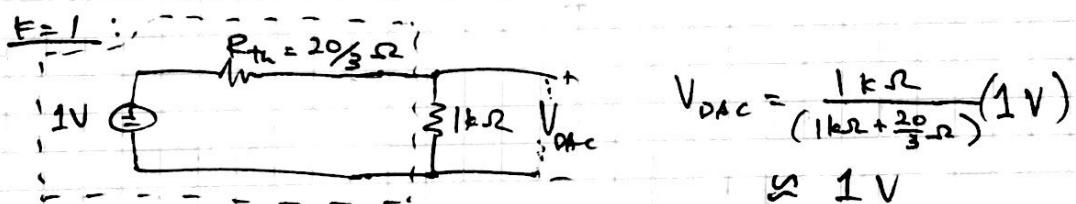and the Thévenin equivalents for $k=1$, $k=2$ are drawn like:




e) Nope

f) Nope.



b) i) $Q_{sc} = C_{sc} V_{init} \rightarrow V_{init} = \frac{Q_{sc}}{C_{sc}}$


$$\left| \frac{dV}{dt} = \frac{1}{C_{sc}} \frac{dQ_{sc}}{dt} = \frac{-I_{load}}{C_{sc}} \right|$$

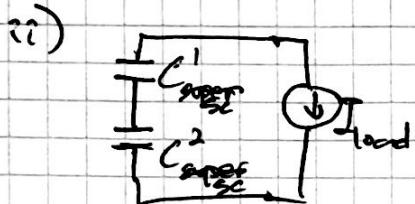

$\frac{dV}{dt} = \frac{-I_{load}}{C_{sc}} dt$

$$\therefore V = \int_{t_0}^t \frac{dV}{dt} = \int_{t_0}^t \frac{-I_{load}}{C_{sc}} dt = \frac{-I_{load}}{C_{sc}} t + V_{init}$$
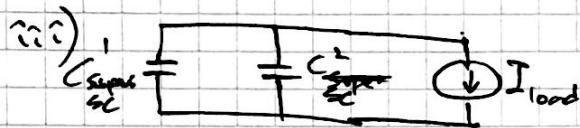
$$\therefore V(t) = \frac{-I_{load}}{C_{sc}} t + V_{init}$$



iii) Since C is parallel, $C_{eff} = 2C_{sc}$

$$V_3(t) \text{ is just } \left| \frac{-I_{load}}{2C_{sc}} t + V_{init} \right|$$

b) ii) $C_{eff} = \frac{C_{sc}^2}{2C_{sc}}$

$$Q_{sc} = C_{eff} V_{init}$$

$$V = \frac{Q_{sc}}{C_{eff}} \rightarrow \frac{dV}{dt} = -\frac{I_{load}}{C_{eff}} \rightarrow dV = -\frac{I_{load}}{C_{eff}} dt$$

$$V(t) = \int dV + V(0) = -\frac{I_{load}}{C_{eff}} dt + V_{init}$$

$$\therefore \boxed{V_2(t) = -\frac{2C_{sc}I_{load}}{C_{sc}^2} t + V_{init}} = -2 \frac{I_{load}}{C_{sc}} t + V_{init}$$

c) i) $V_1(t) = V_{init} - \frac{I_{load}}{C_{sc}} t = V_{min} \rightarrow V_{init} - V_{min} = \frac{I_{load}}{C_{sc}} t$


$$\boxed{t = \frac{C_{sc}}{I_{load}} (V_{init} - V_{min})},$$

ii) $V_2(t) = V_{min} : \boxed{t = \frac{C_{sc}}{2I_{load}} (V_{init} - V_{min})}$

d) I pick config 3, because its lifetime is longer than the others.

iii) $V_3(t) = V_{min} : \boxed{t = \frac{2C_{sc}}{I_{load}} (V_{init} - V_{min})}$

4) DRAM

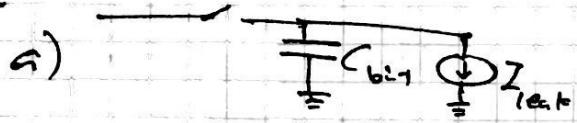

$$C_{bit} = 10^{-15} F$$

$$V_{init} = 1.2 V$$

$$V_{min} \geq 0.8 V$$

$$Q_{init} = C_{bit} V_{init} = (10^{-15})(1.2) = \frac{1.2 \times 10^{-15}}{21.6}$$

$$Q_{min} = C_{bit} V_{min} = \frac{0.8 \times 10^{-15}}{14.4}$$

$$V = \frac{Q_{init}}{C_{bit}} \rightarrow \frac{dV}{dt} = -\frac{I_{leak}}{C_{bit}} \rightarrow dV = -\frac{I_{leak}}{C_{bit}} dt$$

$$V(t) = V_{init} - \frac{I_{leak}}{C_{bit}} t$$

$$V(10^{-3} s) = V_{min}$$

$$V_{init} - \frac{I_{leak}}{C_{bit}} t \Big|_{10^{-3}} = V_{min}$$

~~$$V_{init} - V_{min} = \frac{I_{leak}}{C_{bit}} t \rightarrow t = \frac{C_{bit}}{I_{leak}} (V_{init} - V_{min})$$~~

$$I_{leak} = \frac{C_{bit}}{t} (V_{init} - V_{min})$$

$$I_{leak} = 10 \times \frac{10^{-15} F}{10^{-3} s} (0.4 V)$$

$$\boxed{\begin{aligned} I_{leak} &= 4 \times 10^{-12} A \\ &\boxed{7.2 \times 10^{-12} A} \end{aligned}}$$

b) 1024 DRAM CELLS:

$$L_{col} = 1024 (0.5 \times 10^{-6} m), \quad H_{wire} = 0.5 \times 10^{-6} m$$

$$S = 0.1 \times 10^{-6} m$$

$$C = \frac{\epsilon A}{d}, \quad \epsilon = 8.854 \times 10^{-12} \frac{F}{m}, \quad A = L_{col} \times H_{wire}$$

$$\therefore C = \frac{(8.854 \times 10^{-12} \frac{F}{m})(1024)(0.5 \times 10^{-6} m)(0.5 \times 10^{-6} m)}{0.1 \times 10^{-6} m}$$

$$= \boxed{2.2666 \times 10^{-14} F} = 22.666 fF$$

4) c) Part 1: DRAM Cell has 0 stored — $V_{bit} = 0V$

Since $Q_{bit} = C_{bit} V_{bit}^0 = 0$,
no charge is present, and $\boxed{V_{column} = 0}$

Part 2: DRAM cell has a 1 stored — $V_{bit} = 1.2V$

$$Q_{before} = Q_{after}$$

$$0 + V_{bit} C_{bit} = V_{col} C_{wire} + V_{col} C_{bit} \approx V_{col} (C_{wire} + C_{bit})$$

$$V_{col} = \frac{C_{bit}}{C_{wire} + C_{bit}} V_{bit}$$

$$= \frac{(18 \times 10^{-15} F)}{(20 \times 10^{-15} F) (18 \times 10^{-15} F)} \times (1.2V) = \boxed{0.5684V}$$

d) Assuming $V_{bit} = 1.2V$,

the minimum V_{col} of 0.4V is achieved for some C_{wire}

$$C_{wire} = \frac{C_{bit} V_{bit}}{V_{col}} - C_{bit} = C_{bit} \left(\frac{V_{bit}}{V_{col}} - 1 \right)$$

$$C_{wire} = (18 \times 10^{-15} F) \left(\frac{1.2V}{0.4V} - 1 \right) = \cancel{5.4} \times \cancel{5.4} \times \frac{36}{\cancel{100}} F$$

$$C = \epsilon \frac{A}{d} = \epsilon \frac{H_{wire} \times L_{col}}{S}, \text{ where } H_{wire} = 0.5 \mu m, S = 0.1 \mu m,$$

$$C = \epsilon \frac{(H_{wire})^2 n}{S}$$

$L_{col} = \# \text{ of DRAM cells} \times H_{wire}$

$$\epsilon = 8.854 \times 10^{-12} \frac{F}{m}$$

$$n = \frac{S \cdot C}{\epsilon \cdot H_{wire}^2} = \frac{(0.1 \times 10^{-6} m)(\cancel{5.4} \times 10^{-15} F)}{(8.854 \times 10^{-12} F/m)(0.5 \times 10^{-6} m)^2}$$

$n = 11791.28$ DRAM cells or 11791 cells

$n = 23582.56$ DRAM cells

$n = 1626.38 \rightarrow 1626$ DRAM cells

5) MAG-Lev

a) Btwn T_1 & M: $C_1 = \frac{\epsilon L_{train} \times W}{h}$, $\epsilon = 8.854 \times 10^{-12} \frac{F}{m}$

" T_2 & M: $C_2 = \frac{\epsilon L_{train} \times W}{h}$ " $C_1 = C_2$




~~$C_{eff} = 2 \frac{\epsilon L_{train} \times W}{h}$~~

$C_1 = \frac{\epsilon L_{train} \times W}{h}$ $C_2 = \frac{\epsilon L_{train} \times W}{h}$ $C_{eff} = \frac{C_1 C_2}{C_1 + C_2}$

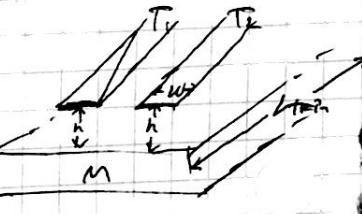c) $C_{eff} = \frac{\epsilon^2 L_{train} \times W^2}{h^2} = \frac{\epsilon L_{train} \times W}{2h}$

$$= \frac{\epsilon}{2} \frac{L_{train} \times W}{h}$$




d) SV - Increase height
OV - Decrease height

$$L_{train} = 100\text{m}$$

$$W = 0.01\text{m}$$

$$C_{eff} = \frac{\epsilon}{2h}$$

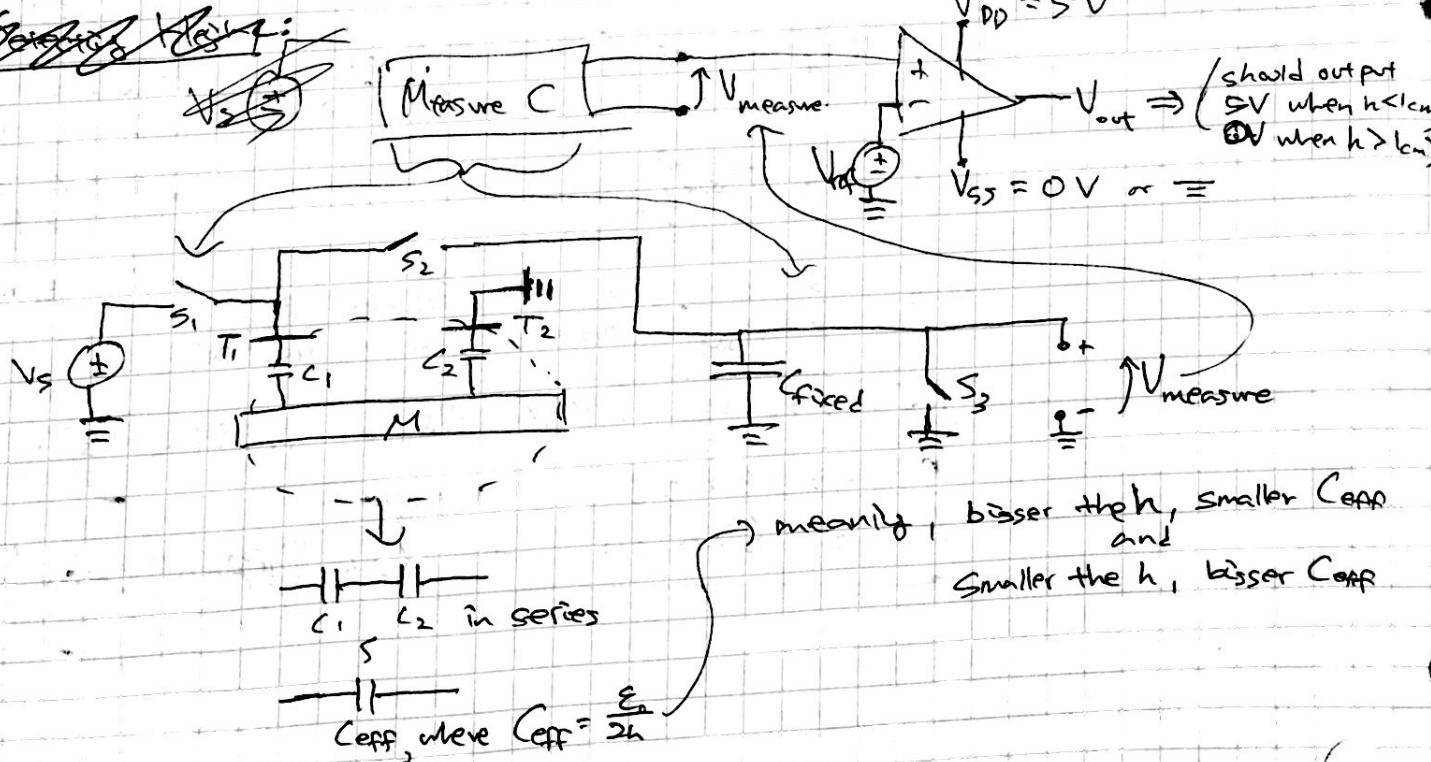

Find V_{ref} s.t. h is @ the ideal height of 0.01m :
 $\epsilon = 8.854 \times 10^{-12} \frac{F}{m}$
 $C_{eff} = 50\epsilon$

$\therefore V_{ref} = \frac{C_{eff}}{C_{eff} + C_{fixed}} V_s$, for any C_{fixed} and $C_{eff} = 50\epsilon F$
 $= 4.42 \times 10^{-10} F$


Redrawing with specific component parts, where we choose

- 1) $C_{fixed} = 50 \epsilon F$ ($\approx 4.42 \times 10^{-10} F$), something relatively similar in magnitude to C_{eff} , so that the extra different $V_{measure}$'s are noticeable.
- 2) $V_s = 5V$.


Then $V_{ref} = \left(\frac{C_{eff}|_{h=0.01m}}{C_{eff}|_{h=0.01m} + C_{fixed}} \right) V_s$

$$V_{ref} = \left(\frac{50 \epsilon F}{100 \epsilon F} \right) V_s = \frac{1}{2} V_s = 2.5V,$$

we have:

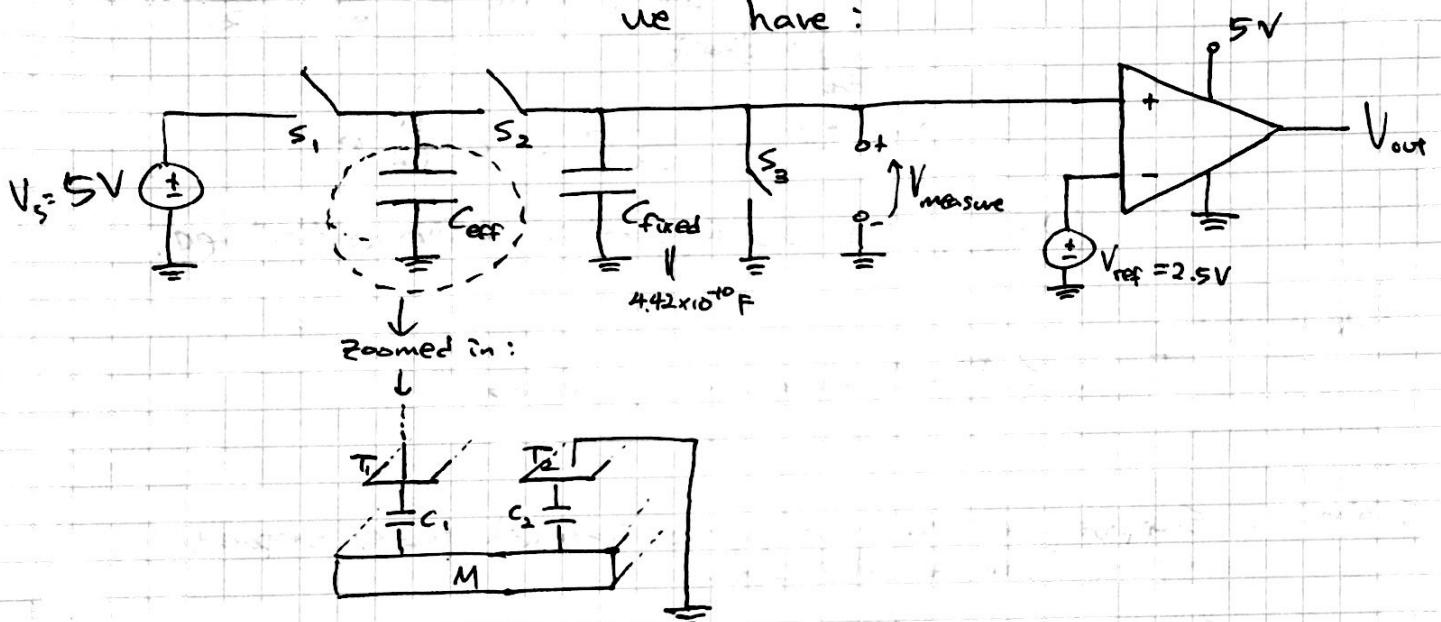

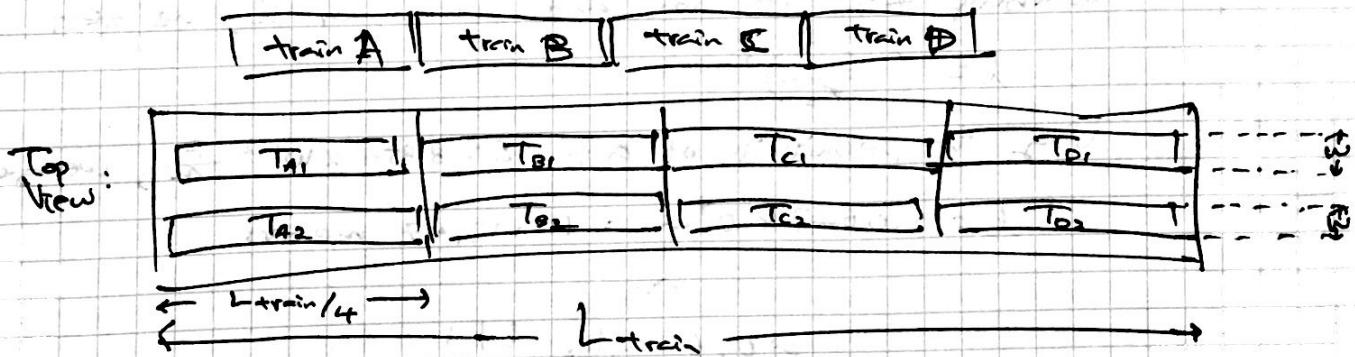e) Separate T_1 & T_2 into 4 different trains.



6) Question: Let there be a circuit consisting of a capacitor & a resistor. The capacitor is charged to an initial voltage V_{init} and has a capacitance of $C = 1 \text{ F}$. Find an expression for its voltage over time.

Solution: $Q = CV \rightarrow V = \frac{Q}{C}$

$$\frac{dV}{dt} = \frac{1}{C} \frac{dQ}{dt}, \text{ since } I = \frac{dQ}{dt}$$

~~$\frac{dV}{dt} = \frac{I}{C}$~~

$$V - IR = \frac{dQ}{dt} R = C \frac{dV}{dt} R$$

Nope, not solving this differential eq.

New Q:

Is a 1 Farad capacitor reasonable?

Solution: Suppose we have two square parallel plates separated by a distance $d = 1 \text{ mm}$.

Capacitance is given by $C = \epsilon \frac{A}{d}$.

For a square plate of length l , $A = l^2$.

Combining those relations and solving for l , we get

$$l = \left(\frac{Cd}{\epsilon_0} \right)^{\frac{1}{2}}$$

Using the permittivity of air $\epsilon = 8.854 \times 10^{-12} \frac{\text{F}}{\text{m}}$, we get

$$l = 1.0627 \times 10^4 \text{ m} = 10627.47 \text{ meters}$$

or

$$\approx 6.6 \text{ miles} !+!$$

Very reasonable.