

EE 16A: Homework 6

David J. Lee
3031796951
dssd1001@berkeley.edu

October 11, 2016

1. Matt Soh 3032109159, William Song 3031799759.

I worked alone for 5 hours then met up with William and Matt to discuss how to approach and solve each problem.

2. Nodal Analysis

- (a) *Solve for all node voltages using nodal analysis. Verify with superposition.*

We would like to compute the node potentials at V_1 and V_2 . So, let us perform nodal analysis by summing the current (flow) that goes in and out of these two nodes.

For V_1 , we have:

$$-1 + \frac{1}{10}(V_1 - 0) + \frac{1}{20}(V_1 - V_2) = 0 \quad (1)$$

which simplifies to

$$\frac{3}{20}V_1 - \frac{1}{20}V_2 = 1. \quad (2)$$

For V_2 , we have:

$$2 + \frac{1}{50}(V_2 - 0) + \frac{1}{20}(V_2 - V_1) = 0 \quad (3)$$

which simplifies to

$$\frac{1}{20}V_1 - \frac{7}{100}V_2 = 2. \quad (4)$$

By putting equations (2) and (4) into the matrix-vector form $Av = b$, we get


$$\begin{bmatrix} \frac{3}{20} & -\frac{1}{20} \\ \frac{1}{20} & -\frac{7}{100} \end{bmatrix} v = \begin{bmatrix} 1 \\ 2 \end{bmatrix} \quad (5)$$

Using ipython notebook to solve for V_1 and V_2 using numpy (code provided in the back), we get

$$\boxed{V_1 = -3.75V} \quad (6)$$

$$\boxed{V_2 = -31.25V} \quad (7)$$

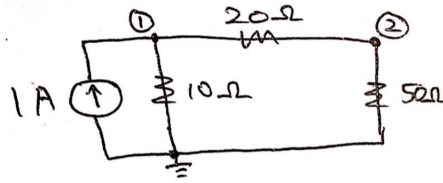
Verifying with superposition: first we consider the left current source (1A):



$$V_1 = IR_{eq} = (1A)\left(\frac{1}{\frac{1}{10\Omega} + \frac{1}{70\Omega}}\right) = \frac{70}{8}V \quad (8)$$

$$V_2 = \left(\frac{50\Omega}{20\Omega + 50\Omega}\right)V_1 = \frac{50}{8}V \quad (9)$$

next, the right current source (2A):

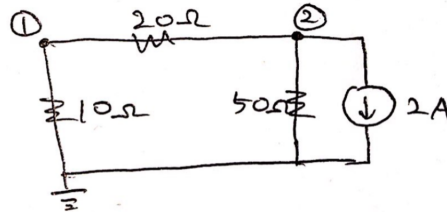

$$V_2 = IR_{eq} = (-2A)\left(\frac{1}{\frac{1}{30\Omega} + \frac{1}{50\Omega}}\right) = -\frac{150}{4}V \quad (10)$$

$$V_1 = \left(\frac{10\Omega}{10\Omega + 20\Omega}\right)V_2 = -\frac{50}{4}V \quad (11)$$


Thus, by adding equations (8) + (11) and (9) + (10) we get

$$V_1 = \frac{70}{8}V - \frac{50}{4}V \Rightarrow \boxed{V_1 = -\frac{15}{4}V} \quad (12)$$

$$V_2 = \frac{50}{8}V - \frac{150}{4}V \Rightarrow \boxed{V_2 = -\frac{125}{4}V} \quad (13)$$

(b) Solve for all node voltages using nodal analysis.

Redraw the circuit with an added node 3:

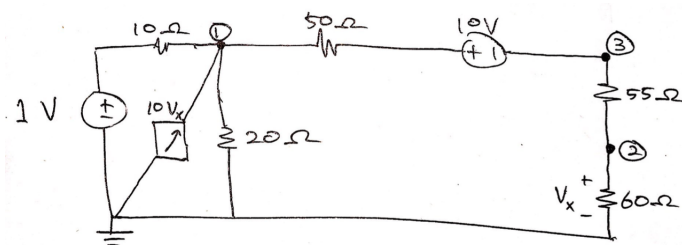

Notice that $V_2 = V_x$ since V_2 is connected to the ground through the 60Ω resistor. Keeping this in mind, we proceed with nodal analysis on each node (1,2,3):

For V_1 , we have:

$$\frac{1}{10\Omega}(V_1 - 1V) - 10V_2 + \frac{1}{20\Omega}(V_1 - 0) + \frac{1}{50\Omega}(V_1 - 10V - v_3) = 0 \quad (14)$$

For V_2 , we have:

$$\frac{1}{60\Omega}(V_2 - 0) + \frac{1}{55\Omega}(V_2 - V_3) = 0 \quad (15)$$

For V_3 , we have:

$$\frac{1}{50\Omega}(V_3 + 10V - V_1) + \frac{1}{55\Omega}(V_3 - V_2) = 0 \quad (16)$$

With some rearranging into the matrix-vector form ($Av = b$, where $v = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$) then solving through iPython(code in the back), we get

$$\boxed{V_1 = 10.402V} \quad (17)$$

$$\boxed{V_2 = 0.146V} \quad (18)$$

3. Thvenin and Norton equivalent circuits

- (a) *Find the Thvenin and Norton equivalent circuits seen from the outside the box.*

First, calculate the effective resistance seen from the voltage source to find the current supplied by the voltage source. The resistances R_3 and R_4 are in series hence have effective resistance of 6Ω . They are connected in parallel to a R_2 resistance yielding an effective resistance of

$$\left(\frac{1}{6} + \frac{1}{3}\right)^{-1} = 2\Omega. \quad (19)$$

This resistance is in series to R_1 , yielding a total effective resistance of

$$R_{eq} = 3\Omega + 2\Omega = 5\Omega. \quad (20)$$

Hence the current supplied by the voltage source is

$$I = \frac{10V}{5\Omega} = 2A \quad (21)$$

Now set up these KCL / KVL equations:

$$-v_2 + v_3 + v_4 = 0 \quad (22)$$

$$v_2 = 3I_2 \quad (23)$$

$$v_3 = 4.5I_3 \quad (24)$$

$$v_4 = 1.5I_3 \quad (25)$$

$$I = I_2 + I_3 = 2A \quad (26)$$

We combine equations (4) through (7) to get

$$\implies -3I_2 + 4.5I_3 + 1.5I_3 = 0 \quad (27)$$

Solving equations (8) and (9) for I_3 , we get

$$3I_3 + 6I_3 = 6A \implies I_3 = \frac{2}{3}A \quad (28)$$

Thus $V_{thvenin} = 4.5I_3 = 3$ Volts. The Norton equivalent is given by

$$I_{norton} = \frac{V_{thvenin}}{R_{thvenin}} = \frac{3}{\frac{9}{4}} = \frac{4}{3}A \quad (29)$$

(b) Find the Thvenin and Norton equivalent circuits seen from the outside the box.


$$V_{thvenin} = IR = (2A)(1.5\Omega) \implies \boxed{V_{th} = 3V} \quad (30)$$

$$I_{sc} = \frac{V_{th}}{(R_1 || R_3 + R_5)} \implies \boxed{I_{no} = 2.8A} \quad (31)$$

$$R_{thvenin} = \frac{V_{th}}{I_{sc}} = \frac{3V}{2.8A} \implies \boxed{R_{th} = 1.0714\Omega} \quad (32)$$

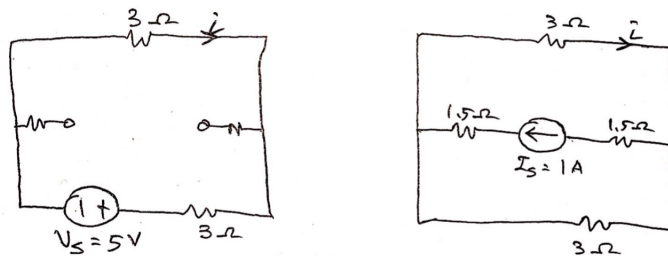4. **Nodal Analysis Or Superposition?** Solve for the current through the 3Ω resistor, marked as i , using superposition. Verify using nodal analysis. You can use IPython to solve the system of equations if you wish. Where did you place your ground, and why?

Using superposition: We look at one independent source at a time, and in this case, V_s then I_s :



From the left superposition, we can easily see that

$$I = \frac{V}{R_{eq}} = \frac{5V}{3\Omega + 3\Omega} = \frac{5}{6}A \quad (33)$$

and since i is just in the opposing direction of the same current,

$$i = -I = -\frac{5}{6}A \quad (34)$$


From the right superposition, we notice the symmetry so it is easy to see that the current source splits evenly:

$$i = \frac{1}{2}I_s = \frac{1}{2}A \quad (35)$$

Thus by superposition,

$$i = -\frac{5}{6}A + \frac{1}{2}A \Rightarrow \boxed{i = -\frac{1}{3}A} \quad (36)$$

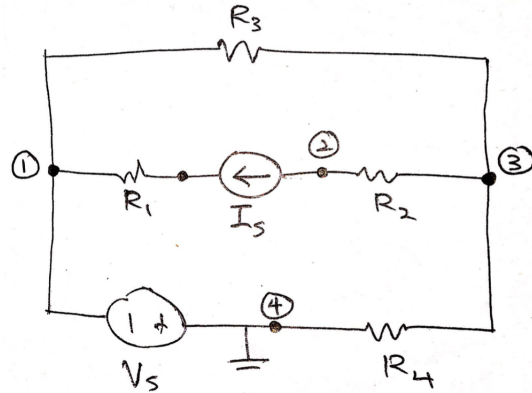Verify using nodal analysis: From all the nodes that exist in this circuit, we label nodes 1, 2, 3, and 4, and recognizing that we cannot solve for all of these potentials, we place a ground node to set the potential of $V_4 = 0$:



It is easy to see that V_1 (potential at node 1) is

$$V_1 = -V_s \quad (37)$$

Now, proceed with nodal analysis on nodes 2 and 3:

For V_2 , we have:

$$I_s + G_2(V_3 - V_4) = 0 \quad (38)$$

For V_3 , we have:

$$G_3(V_4 - V_1) + G_2(V_4 - V_3) + G_4(V_4 - 0) = 0 \quad (39)$$

Substituting in V_1 in equation (36) then rearranging into the matrix-vector form ($Av = b$, where $v = \begin{bmatrix} V_2 \\ V_3 \end{bmatrix}$) then solving through iPython(code in the back), we get

$$V_2 = -5.5V \quad (40)$$

$$V_3 = -4V \quad (41)$$

Finally, to solve for current i through R_3 ,

$$i = \frac{\Delta V}{R_3} = \frac{V_1 - V_3}{R_3} = \frac{-5V - (-4V)}{3\Omega} \Rightarrow \boxed{i = -\frac{1}{3}A} \quad (42)$$

5. Optional


6. Solving Circuits with Voltage Sources

- (a) What relationship does the voltage source enforce between v_1 and v_4 ?

$$\boxed{v_1 - v_4 = V_s} \quad (43)$$

The voltage source fixes the nodes to be a constant offset from each other.

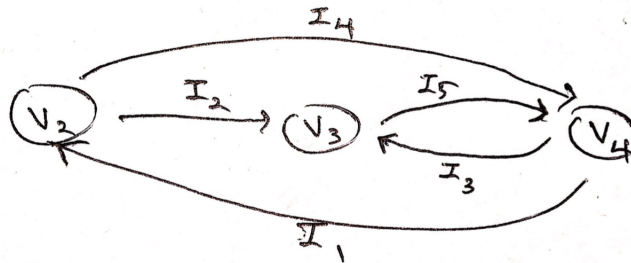- (b) Draw the graph for the circuit where v_1 and v_4 are combined into one node. Specify a new incidence matrix for this graph.



$$F = \begin{bmatrix} -1 & 0 & 1 \\ 1 & -1 & 0 \\ 0 & -1 & 1 \\ 1 & 0 & -1 \\ 0 & 1 & -1 \end{bmatrix}$$

- (c) Find R and \vec{b} so that Ohms law is written $F\vec{v} + \vec{b} = R\vec{i}$.

$$R = \begin{bmatrix} R_1 & 0 & 0 & 0 & 0 \\ 0 & R_2 & 0 & 0 & 0 \\ 0 & 0 & R_3 & 0 & 0 \\ 0 & 0 & 0 & R_4 & 0 \\ 0 & 0 & 0 & 0 & R_5 \end{bmatrix}$$

$$\vec{b} = \begin{bmatrix} V_s \\ 0 \\ V_s \\ 0 \\ 0 \end{bmatrix}$$

- (d) What is \vec{f} in this circuit? write \vec{v} in terms of known quantities ($\vec{f}, \vec{b}, G, F, R$). You may need to modify several of the members of the derived equation by grounding a node and dropping a row or a column in order to give the problem a unique solution.

First let us compute the product $F^T \vec{i}$:

$$\begin{bmatrix} -1 & 1 & 0 & 1 & 0 \\ 0 & -1 & -1 & 0 & 1 \\ 1 & 0 & 1 & -1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} -i_1 + i_2 + i_4 \\ -i_2 - i_3 + i_5 \\ i_1 + i_3 - i_4 - i_5 \end{bmatrix}$$

From this, we know the vector \vec{f} has 3 elements in it. Furthermore, we know we combined the nodes 1 and 4 into a supernode. Therefore:

$$\vec{f} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} \quad (44)$$

Solving the Ohms law equation for \vec{i} ,

$$\vec{i} = G(F\vec{v} + \vec{b}).$$

Now plugging this expression into KCL we see

$$F^T G(F\vec{v} + \vec{b}) = -\vec{f}$$

Does this equation have a unique solution? Let us first go back to the matrix F , row-reducing we see F has a linearly dependent column.

$$F = \begin{bmatrix} -1 & 0 & 1 \\ 1 & -1 & 0 \\ 0 & -1 & 1 \\ 1 & 0 & -1 \\ 0 & 1 & -1 \end{bmatrix} \rightarrow \begin{bmatrix} 1 & 0 & -1 \\ 0 & 1 & -1 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

This implies that the system is underdetermined. In order to make this system determined, we can drop one column of the F matrix, and ignore one potential in \vec{v} . We will assign this node a potential of 0. This is equivalent to grounding a node in a circuit (\vec{v}_{gr}).

Call the new matrix F_{gr} and the new \vec{f} as \vec{f}_{gr} . Then F_{gr} has no null space and:

$$\vec{i} = GF_{gr}\vec{v}_{gr} + G\vec{b} \quad (45)$$

Plugging this into KCL again, we see

$$F_{gr}^T GF_{gr}\vec{v}_{gr} + F_{gr}^T G\vec{b} = -\vec{f}_{gr} \quad (46)$$

Thus,

$$F_{gr}^T GF_{gr}\vec{v}_{gr} = -\vec{f}_{gr} - F_{gr}^T G\vec{b} \quad (47)$$

(e) write \vec{i} in terms of known quantities

$$\vec{i} = G(F_{gr}\vec{v}_{gr} + \vec{b}) \quad (48)$$

(f) See iPython Notebook in the end of PDF