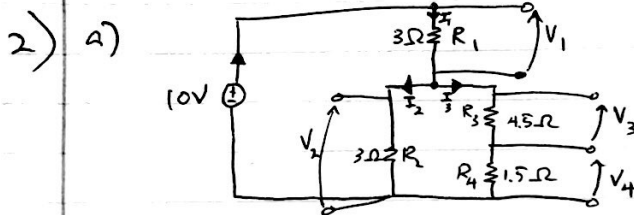


- 1) Matthew Soh - 3032109159  
William Song - 3031799759

I worked alone for about 3 hours - less this time around b/c of time constraints - and discussed with group on Sunday.



Ohm's Law:

$$V_1 = 3 I_1$$

$$V_2 = 3 I_2$$

$$V_3 = 4.5 I_3$$

$$V_4 = 1.5 I_3$$

applying KVL multiple times we get:

$$V_2 = V_3 + V_4$$

$$V_1 + V_2 = 10$$

$$V_1 + V_3 + V_4 = 10$$

applying KCL on the junction we get:



$$I_1 = I_2 + I_3$$

Combining the three sets of equations, we get:

$$3 I_2 - 4.5 I_3 - 1.5 I_3 = 0$$

$$3 I_1 + 3 I_2 = 10$$

$$3 I_1 + 4.5 I_3 + 1.5 I_3 = 10$$

$$I_1 - I_2 - I_3 = 0$$

Solving for the currents, we get:

$$\begin{bmatrix} 0 & 3 & -6 & | & 0 \\ 3 & 3 & 0 & | & 10 \\ 3 & 0 & 6 & | & 10 \\ 1 & -1 & -1 & | & 0 \end{bmatrix} \rightsquigarrow \begin{bmatrix} 1 & 0 & 0 & | & 2 \\ 0 & 1 & 0 & | & \frac{4}{3} \\ 0 & 0 & 1 & | & \frac{2}{3} \\ 0 & 0 & 0 & | & 0 \end{bmatrix}$$

$$\therefore \begin{cases} I_1 = 2 \text{ A} \\ I_2 = \frac{4}{3} \text{ A} \\ I_3 = \frac{2}{3} \text{ A} \end{cases}$$

We can now solve for the voltages across the resistors by plugging in the  $I_1, I_2, I_3$  into the Ohm's Law equations:


$$\begin{aligned} V_1 &= 3 I_1 = 3(2) = 6 \text{ V} \\ V_2 &= 3 I_2 = 3\left(\frac{4}{3}\right) = 4 \text{ V} \\ V_3 &= 4.5 I_3 = 4.5\left(\frac{2}{3}\right) = 3 \text{ V} \\ V_4 &= 1.5 I_3 = 1.5\left(\frac{2}{3}\right) = 1 \text{ V} \end{aligned}$$

Thus, the voltages across and currents flowing through each resistor is given by:

$$\begin{array}{ll} R_1: 6 \text{ V}, 2 \text{ A} & R_3: 3 \text{ V}, \frac{2}{3} \text{ A} \\ R_2: 4 \text{ V}, \frac{4}{3} \text{ A} & R_4: 1 \text{ V}, \frac{2}{3} \text{ A} \end{array}$$

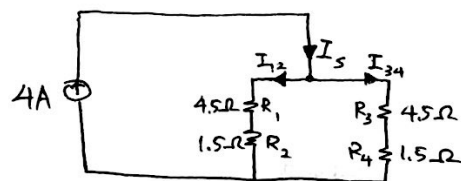b) Disregarding  $R_5$ , we can see that  $(R_1 + R_2)$  parallels and is symmetrical to  $(R_3 + R_4)$ . Thus we can safely analyze the circuit as if  $R_5$  wasn't there.

Also, the symmetry tells us that  $I_5 = 4 \text{ A}$  splits at the first junction evenly and  $I_{12} = I_{34} = 2 \text{ A}$ :




Voltages across each resistor now can be calculated easily applying Ohm's Law,

$$\begin{aligned} V_1 &= I_{12} R_1 = 2(4.5) = 9 \text{ V} = V_1 \\ V_2 &= I_{12} R_2 = 2(1.5) = 3 \text{ V} = V_2 \\ V_3 &= I_{34} R_3 = 2(4.5) = 9 \text{ V} = V_3 \\ V_4 &= I_{34} R_4 = 2(1.5) = 3 \text{ V} = V_4 \end{aligned}$$

And simply,  $V_5 = 0$

3) a)

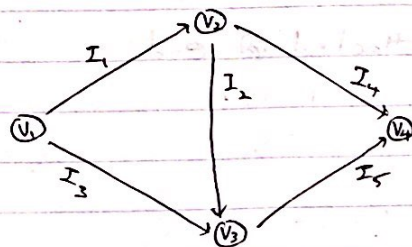

$$F = \begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & 1 & -1 & 0 \\ 1 & 0 & -1 & 0 \\ 0 & 1 & 0 & -1 \\ 0 & 0 & 1 & -1 \end{bmatrix}$$

b) Let  $\vec{v}$  represent the voltage nodes.

$$F\vec{v} = \begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & 1 & -1 & 0 \\ 1 & 0 & -1 & 0 \\ 0 & 1 & 0 & -1 \\ 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} v_1 - v_2 \\ v_2 - v_3 \\ v_1 - v_3 \\ v_2 - v_4 \\ v_3 - v_4 \end{bmatrix} \text{ is a vector of } \Delta V, \text{ the voltage differences.}$$

since  $R = \begin{bmatrix} R_1 & & & \\ & R_2 & & \\ & & R_3 & \\ & & & R_4 \\ & & & & R_5 \end{bmatrix}$  is the diagonal matrix of branch matrices and  $\vec{i} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}$  the current vector,

We can rewrite the Ohm's Law ( $V=IR$ ) as:

$$F\vec{v} = R\vec{i}$$

c) First, taking  $F\vec{v} = R\vec{i}$  and solving for  $\vec{i}$ , also,  $f = \begin{bmatrix} -i \\ 0 \\ 0 \\ 0 \\ i \end{bmatrix}$   
 $\vec{i} = R^{-1}F\vec{v}$ .

We know that  $R$ , the diagonal matrix, is invertible, and  $R^{-1} = G$  where  $G$  is the conductance matrix. So we can write  $\vec{i} = GF\vec{v}$ .

Now, using  $F^T\vec{i} + f = 0$ , we can write  $\vec{v}$  in terms of known quantities by plugging in  $\vec{i}$ :

$$\boxed{F^T G F \vec{v} = -f} \text{ which is in the form } Ax = b, \text{ so } \vec{v} \text{ can be solved.}$$

d) Solving for  $\vec{i}$  from the rewritten Ohm's Law,

$$\vec{i} = GF\vec{v}. \text{ Then using the above } \vec{v},$$

$$\vec{i} = G F (F^T G F)^{-1} f = -G F F^{-1} G^{-1} F^T^{-1} f$$

$$\boxed{\vec{i} = -F^T^{-1} f}$$

e) See IPython Notebook attached @ end.



4) a)  $P = IV \rightarrow I = \frac{P}{V} = \frac{0.4 \text{ W}}{3.8 \text{ V}} \approx 0.1053 \text{ Amps}$

Assume the Galaxy S3's average power draw rate is 0.1053 Amps.

Then a full charge of 2200 mAh would last:

$$\frac{2200 \text{ mAh}}{105.2632 \text{ mA}} = \boxed{20.9 \text{ hours}}$$

b) Energy for full charge:

$$0.4 \frac{\text{J}}{\text{s}} \times 20.9 \text{ hr} \times \frac{3600 \text{ s}}{1 \text{ hr}} = \boxed{30,096 \text{ J}}$$

which is  $\frac{30096 \text{ J}}{3.8 \text{ V}} = \boxed{7,920 \text{ Charge}}$

c) For a month of 31 days:


$$\$0.16 / \text{kWh} \times \frac{1 \text{ kWh}}{10^3 \text{ Wh}} \times 3.8 \text{ V} \times 2.2 \text{ Ah} \times 31 = \boxed{\$0.040128}$$

d) In 16 hours, you get  $16 \text{ h} \times 40 \text{ mA} = 640 \text{ mAh}$ , which is not enough.

How many cells?  $2200 \text{ mAh} \times \frac{1}{40 \text{ mA}} \times 3.8 \text{ V} \times \frac{1}{0.5 \text{ V}} = \boxed{418 \text{ cells}}$

$\$1.50 \times \frac{1}{0.2 \text{ W}} \times 16 \text{ hr} \times 365 \times 60 \times 60 \times 10 = \boxed{\$0.00000570776 / \text{J}}$

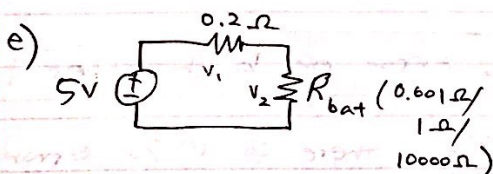This is a very silly idea. Who wants the hassle?



$$S = V_1 + V_2; V_1 = 0.2 I, V_2 = R_{bat} I$$

$$S = 0.2 I + R_{bat} I$$

$$I = \frac{S}{0.2 + R_{bat}}$$

@  $R_{bat} = 0.001 \Omega$ :  $I = 24.87562 \text{ A}$ ,  $P = I^2 R = 0.6188 \text{ W}$ ,

Time to Charge =  $8.6 / 0.61 \approx 13.5 \text{ hr}$

@  $R_{bat} = 1 \Omega$ :  $I = 4.1666 \text{ A}$ ,  $P = I^2 R = 17.361 \text{ W}$ ,

Time to Charge =  $0.48 \text{ hr}$

@  $R_{bat} = 10000 \Omega$ :  $I = 0.00049990 \text{ A}$ ,  $P = I^2 R = 0.00249990 \text{ W}$ ,

Time to Charge  $\approx 139 \text{ days}$

- 5) a) Similar to question 2) b), we can see that if the current across the galvanometer is 0, the circuit must be symmetrical, and  $(R_1 + R_2)$  be parallel to  $(R_3 + R_x)$ , and  $I$  splits evenly to each parallel branch.

The total resistance can be written as

$$R_{eq} = \frac{1}{\frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_x}} = \frac{1}{\frac{R_1 + R_2 + R_3 + R_x}{(R_1 + R_2)(R_3 + R_x)}}$$

$$R_{eq}(R_1 + R_2 + R_3 + R_x) = R_1 R_3 + R_1 R_x + R_2 R_3 + R_2 R_x$$

or,

$$\text{Since } V = I R_{eq} \Rightarrow R_{eq} = \frac{V}{I},$$

$$\boxed{\frac{I}{V} = \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_x}}$$

- b) The maximum for  $R_x$  is  $\boxed{250 \Omega}$

- c) Procedure: Subtract  $R_x$  by  $100 \Omega$ , and multiply by the inverse of the temperature coefficient of PT100:

$$\text{Temperature of } R_x (^{\circ}\text{C}) = (R_x - 100) \times \frac{1^{\circ}\text{C}}{0.366 \Omega} = \frac{R_x - 100}{0.366}$$

Maximum temp would be @ the max  $R_x$ , which is


$$\frac{250 - 100}{0.366} \approx \boxed{409.8361^{\circ}\text{C}}$$

- d)  $\left( \frac{430.5 - 410}{410} \right) \times 100\% = \boxed{5\% \text{ error on both sides}}$

- e) With the 5% max error in  $R_3$ , there is 10% error in  $R_1$  ( $\frac{5}{50} = 0.1$ ).  $\boxed{10\%}$

- f) Not very accurate for sure!

6) a)  $R = 8000 \Omega$

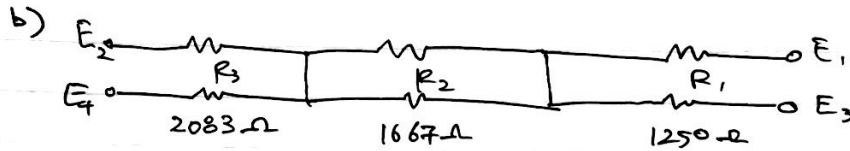

c) Across  $E_4 - E_3$  :

$R_{eq} = R_1 + R_3 + \frac{R_2}{2}$

$$\therefore V_{E_4 - E_3} = I R_{eq} = \boxed{4.167 V} = 4.167 V$$

d)  $R_{eq} = R_{plate} \left( \frac{V_1}{H} + \frac{V_2 - V_1}{2H} + \frac{H - V_2}{H} \right)$

$$V = I R_{plate} \left( \frac{V_1}{H} + \frac{V_2 - V_1}{2H} + \frac{H - V_2}{H} \right)$$

$$\Rightarrow V_2 - V_1 = 2H \left( 1 - \frac{V}{I R_{plate}} \right)$$

$\therefore$  It is easy to see that this gives us the information about the difference in height of the two touch positions.

# HW5 Q3

## EECS 16A: Designing Information Devices and Systems I, Fall 2016

### Circuit solver

In this question we will write a program that solves circuits methodically.

```
In [89]: import numpy as np
         from numpy import linalg
         from __future__ import print_function
```

(i) Write the incidence matrix  $F$  for the graph.

```
In [90]: F = np.matrix([[1, -1, 0, 0],
                        [0, 1, -1, 0],
                        [1, 0, -1, 0],
                        [0, 1, 0, -1],
                        [0, 0, 1, -1]])
         print('\nF:\n',F)
```

```
F:
[[ 1 -1  0  0]
 [ 0  1 -1  0]
 [ 1  0 -1  0]
 [ 0  1  0 -1]
 [ 0  0  1 -1]]
```

(ii) Specify the resistance matrix  $R$ .



```
In [91]: R1, R2, R3, R4, R5 = 100000, 200, 100, 100000, 100
R = np.matrix([[R1,0,0,0,0],
               [0,R2,0,0,0],
               [0,0,R3,0,0],
               [0,0,0,R4,0],
               [0,0,0,0,R5]])

# For convenience, we will define the conductance matrix G as the inverse
G = np.linalg.inv(R)

print('\nR:\n',R)
print('\nG:\n',G)
```

```
R:
[[100000      0      0      0      0]
 [      0    200      0      0      0]
 [      0      0    100      0      0]
 [      0      0      0 100000      0]
 [      0      0      0      0    100]]

G:
[[ 1.00000000e-05  0.00000000e+00  0.00000000e+00  0.00000000e+00
  0.00000000e+00]
 [ 0.00000000e+00  5.00000000e-03  0.00000000e+00  0.00000000e+00
  0.00000000e+00]
 [ 0.00000000e+00  0.00000000e+00  1.00000000e-02  0.00000000e+00
  0.00000000e+00]
 [ 0.00000000e+00  0.00000000e+00  0.00000000e+00  1.00000000e-05
  0.00000000e+00]
 [ 0.00000000e+00  0.00000000e+00  0.00000000e+00  0.00000000e+00
  1.00000000e-02]]
```

(iii) Write down the vector  $f$  so that KCL is satisfied as:  $F^T i + f = 0$

```
In [92]: I = 3
f = np.array([[ -I],
              [ 0],
              [ 0],
              [ I]])
print('\nf:\n', f)
```

```
f:
[[-3]
 [ 0]
 [ 0]
 [ 3]]
```

(iv) Setting a potential in  $v$  to 0 corresponds to deleting a column of  $F$ . Write down our new "grounded"

```
In [93]: F_grounded = np.delete(F, np.s_[0:1] ,1)
f_1 = np.delete(f, 0, 0)
print('\nF_grounded:\n', F_grounded)
```

```
F_grounded:
[[-1  0  0]
 [ 1 -1  0]
 [ 0 -1  0]
 [ 1  0 -1]
 [ 0  1 -1]]
```

(v) Implement your algebraic solution to compute  $v$  in terms of  $F_{\text{grounded}}$ ,  $G$ , and  $f$ .

Hint: if you have an equation  $Av=b$  where  $A$  is a square matrix and  $b$  is a vector, use `np.linalg.solve`

```
In [94]: A = np.dot(F_grounded.T, np.dot(G,F_grounded))
v = np.linalg.solve(A,-f_1)
print('\nv:\n', v)
```

```
v:
[[-299.7002997]
 [-299.7002997]
 [-599.4005994]]
```

(vi) Compute  $\vec{i}$  with your solution of  $\vec{v}$ .

```
In [96]: i = np.linalg.solve(F.T, -f)
```

```
print('\ni:\n', i)
```

```
-----  
LinAlgError                                Traceback (most recent call last  
<ipython-input-96-8d19665f8ca0> in <module>()  
----> 1 i = np.linalg.solve(F.T, -f)  
      2  
      3 print('\ni:\n', i)
```

```
/Users/Dawvid/anaconda3/lib/python3.4/site-packages/numpy/linalg/linalg.py  
    353     a, _ = _makearray(a)  
    354     _assertRankAtLeast2(a)  
--> 355     _assertNdSquareness(a)  
    356     b, wrap = _makearray(b)  
    357     t, result_t = _commonType(a, b)
```

```
/Users/Dawvid/anaconda3/lib/python3.4/site-packages/numpy/linalg/linalg.py  
(*arrays)  
    210     for a in arrays:  
    211         if max(a.shape[-2:]) != min(a.shape[-2:]):  
--> 212             raise LinAlgError('Last 2 dimensions of the array must  
    213  
    214 def _assertFinite(*arrays):
```

```
LinAlgError: Last 2 dimensions of the array must be square
```

```
In [ ]:
```