

# prob6

October 11, 2016

## 1 HW6 Q6

1.0.1 EECS 16A: Designing Information Devices and Systems I, Fall 2016

## 2 Circuit solver

In this question we will write a program that solves circuits methodically, able to include both voltage and current sources.

```
In [29]: import numpy as np
         from numpy import linalg
         from __future__ import print_function
```

(i) Write the incidence matrix  $F$  for the graph, considering  $v_1$  and  $v_4$  as a combined “supernode”.

```
In [30]: F = np.array([[ -1, 0, 1],
                       [ 1, -1, 0],
                       [ 0, -1, 1],
                       [ 1, 0, -1],
                       [ 0, 1, -1]])
         print('\nF:\n',F)
```

```
F:
[[-1  0  1]
 [ 1 -1  0]
 [ 0 -1  1]
 [ 1  0 -1]
 [ 0  1 -1]]
```

(ii) Specify the resistance matrix  $R$  and the vector of voltage sources  $\vec{b}$ .

```
In [31]: R1,R2,R3,R4,R5 = 100000, 200, 100, 100000, 100
         Rvec = np.array([R1,R2,R3,R4,R5])
         R = np.eye(5)*Rvec

         Vs = 10
         b = np.array([[Vs],[0],[Vs],[0],[0]])

         # For convenience, we will define the conductance matrix G as the inverse of R.
         G = np.linalg.inv(R)

         print('\nR:\n',R)
         print('\nb:\n',b)
```

```
R:
[[ 100000.    0.    0.    0.    0.]
 [    0.   200.    0.    0.    0.]
 [    0.    0.   100.    0.    0.]
 [    0.    0.    0. 100000.    0.]
 [    0.    0.    0.    0.   100.]]
```

```
b:
[[10]
 [ 0]
 [10]
 [ 0]
 [ 0]]
```

(iii) Write down the vector  $f$  so that KCL is satisfied as:  $F^T i + f = 0$

```
In [32]: f = np.array([[0],[0],[0]])
         print('\nf:\n', f)
```

```
f:
[[0]
 [0]
 [0]]
```

(iii) What is the rank of  $F$ ? Does it have a null space? If so, what is it?

Row-reducing  $F$ , we see  $F$  has a linearly dependent column (see Problem 6 Part d). Therefore,  $\text{rank}(F)$  is 2.

Since it's not a full rank,  $F$  does have a null space.

The null space is spanned by  $[[1],[1],[1]]$ .

```
In [33]: # any code you write to help you answer above
```

```
from sympy import Matrix
Fm = Matrix(F)

# Frr = row-reduced F matrix
Frr = Fm.rref()
print(Frr)

# Fns = nullspace of F
Fns = Fm.nullspace()
print(Fns)
```

```
(Matrix([
[1.0, 0, -1.0],
[ 0, 1.0, -1.0],
[ 0, 0, 0],
[ 0, 0, 0],
[ 0, 0, 0]]), [0, 1])
[Matrix([
[1.0],
[1.0],
[ 1]]])]
```

(iv) Setting a potential in  $v$  to 0 corresponds to deleting a column of  $F$ . Let  $v_4 = 0$ , and write down our new “grounded” matrix  $F$ :  $F_{\text{grounded}}$

```
In [34]: F_grounded = F[:, :2]
         print('\nF_grounded:\n', F_grounded)
```

```
F_grounded:
[[-1  0]
 [ 1 -1]
 [ 0 -1]
 [ 1  0]
 [ 0  1]]
```

(v) Implement your algebraic solution to compute  $v$  in terms of  $F$ ,  $G$ ,  $\vec{f}$ , and  $\vec{b}$ . You may also have to slice  $\vec{f}$  and  $\vec{b}$ .

```
In [35]: A = np.dot(F_grounded.T, np.dot(G, F_grounded))
         print('\nA:\n', A)

         B = np.linalg.inv(A)
         print('\nB:\n', B)

         f_gr = f[0:2]

         v_gr = - B.dot(f_gr + np.dot(F_grounded.T, np.dot(G, b)))
         print('\nv:\n', v_gr)
```

```
A:
[[ 0.00502 -0.005 ]
 [-0.005   0.025 ]]
```

```
B:
[[ 248.75621891  49.75124378]
 [ 49.75124378  49.95024876]]
```

```
v:
[[ 5.]
 [ 5.]]
```

(vi) Compute  $\vec{i}$  with your solution of  $\vec{v}$ .

```
In [36]: i = G.dot(np.dot(F_grounded, v_gr) + b)

         print('\ni:\n', i)
```

```
i:
[[ 5.00000000e-05]
 [ 8.88178420e-18]
 [ 5.00000000e-02]
 [ 5.00000000e-05]
 [ 5.00000000e-02]]
```

```
In [ ]:
```